

<http://DrSatvir.in>



LINEAR INTEGRATED CIRCUITS

DR SATVIR SINGH
DEPARTMENT OF ECE
IKG PUNJAB TECHNICAL UNIVERSITY
KAPURTHALA - 144603 (PB) INDIA



Do Like &
Subscribe

<http://DrSatvir.in>

LINEAR INTEGRATED CIRCUITS

Part-01: Differential Amplifier




Do Like &
Subscribe

Differential Amplifier


1. Differential Amplifier amplifies the difference between two input voltages.
2. These two inputs are
 - Inverting Input Terminal
 - Non-Inverting Input Terminal
3. It also suppresses any common voltage (noise) applied at both input terminals.

$$V_o = A_d(V_+ - V_-)$$

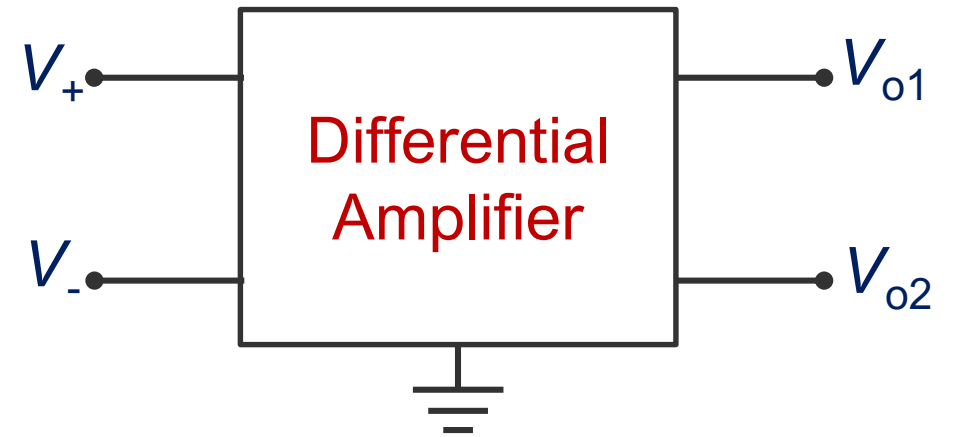


Differential Amplifier Structure

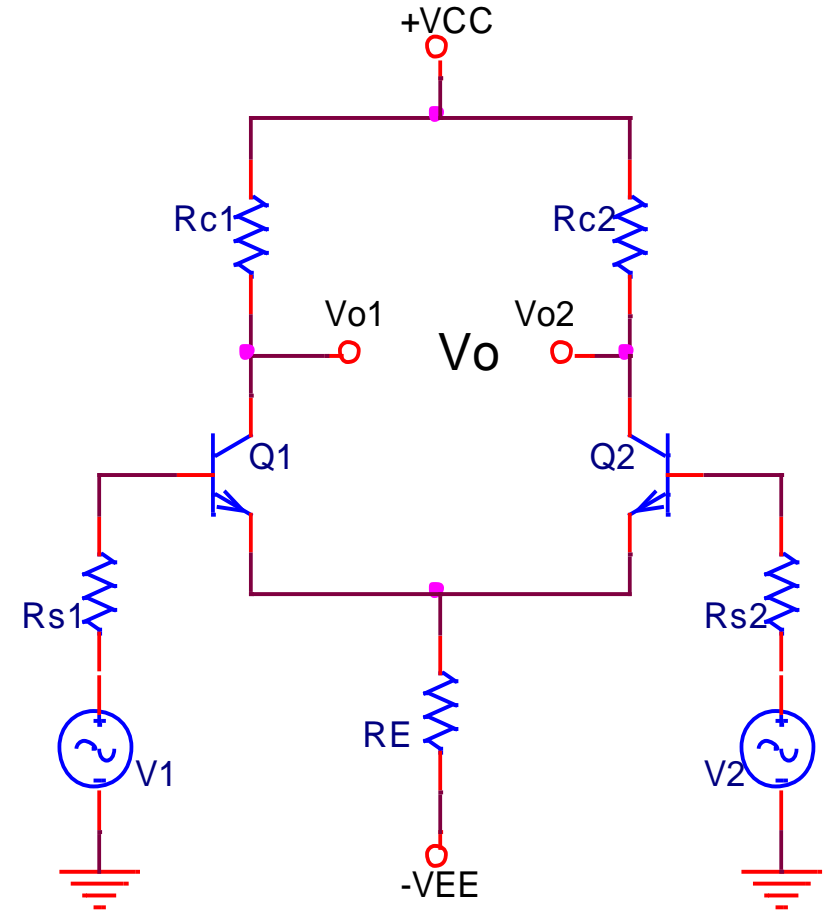- ❑ Two identical transistor
- ❑ Two biasing supplies voltages
 $+V_{CC}$ and $-V_{EE}$
- ❑ Inputs applied at BJT base terminals
- ❑ Output obtained from collector terminals




Types of Differential Amplifier

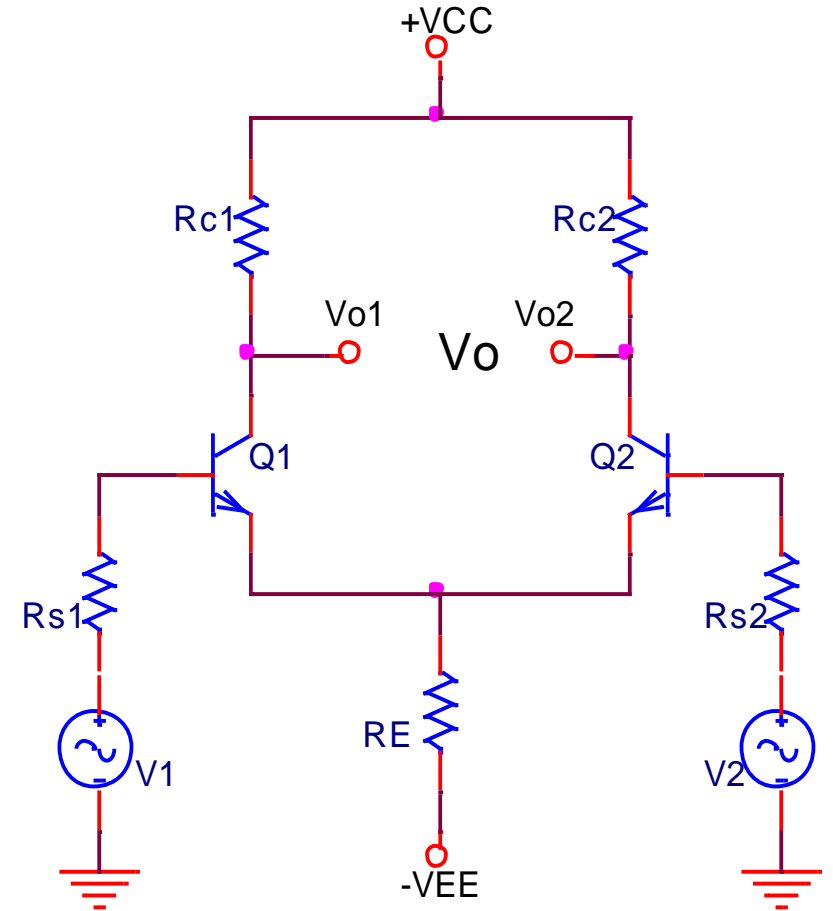1. Dual Input Balanced Output
2. Dual Input Unbalanced Output
3. Single-input Balanced Output
4. Single-input Unbalanced Output




Types of Differential Amplifier

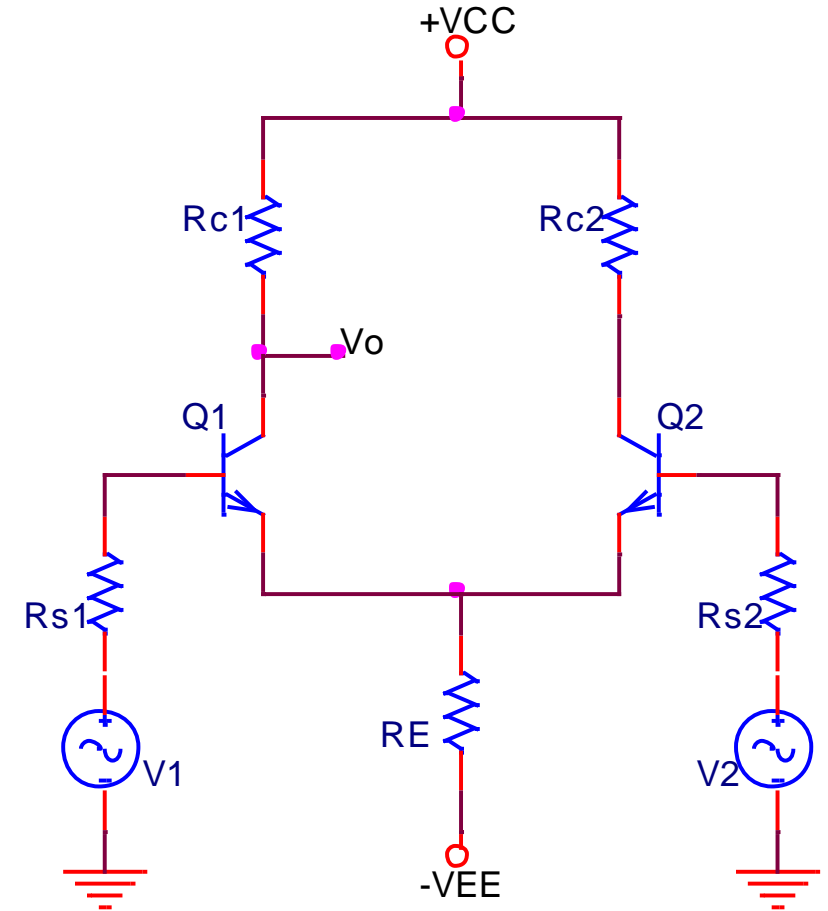1. Dual Input Balanced Output
2. Dual Input Unbalanced Output
3. Single-input Balanced Output
4. Single-input Unbalanced Output



Types of Differential Amplifier

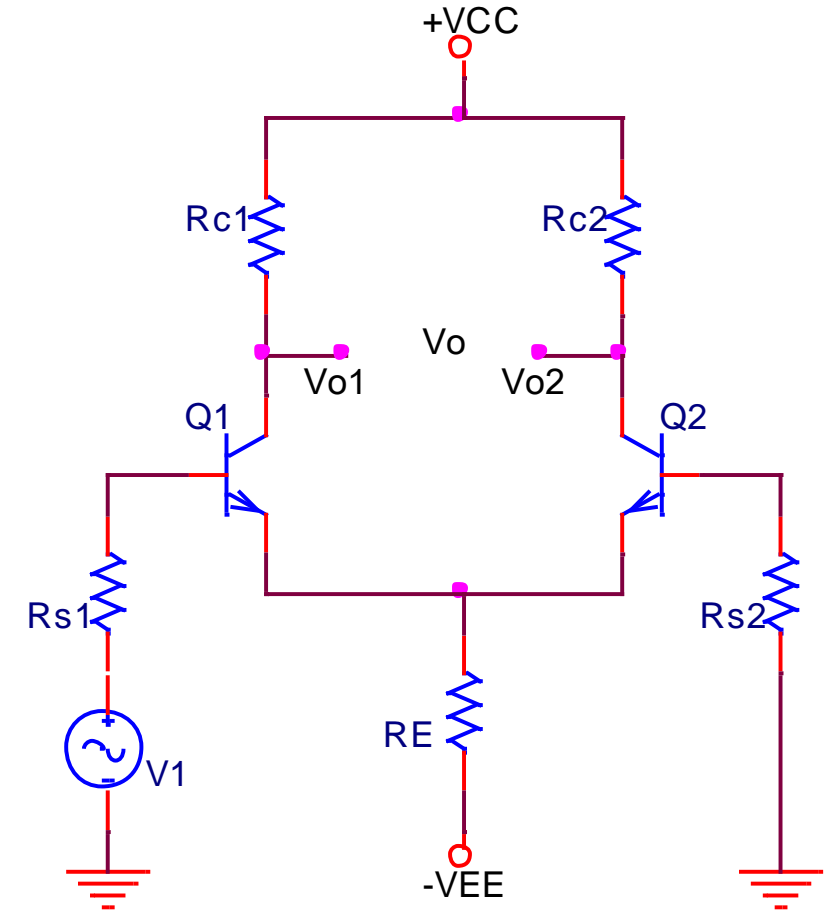1. Dual Input Balanced Output
2. Dual Input Unbalanced Output
3. Single-input Balanced Output
4. Single-input Unbalanced Output



Types of Differential Amplifier

1. Dual Input Balanced Output
2. Dual Input Unbalanced Output
3. Single-input Balanced Output
4. Single-input Unbalanced Output

