

<http://DrSatvir.in>



# LINEAR INTEGRATED CIRCUITS

**DR SATVIR SINGH**  
DEPARTMENT OF ECE  
IKG PUNJAB TECHNICAL UNIVERSITY  
KAPURTHALA - 144603 (PB) INDIA



Do Like &  
Subscribe

<http://DrSatvir.in>

---

# LINEAR INTEGRATED CIRCUITS

**Part-02:** Mathematical Analysis of  
OpAmp based Differential Amplifier



Do Like &  
Subscribe


---

# Differential Amplifier

A Differential Amplifier is a type of **electronic amplifier** that **amplifies the difference** between **two input voltages**. It also suppresses any common voltage (e.g. noise) present at both Inverting & Non-inverting input terminals.

Mathematically,

$$V_o = A_d(V_+ - V_-)$$

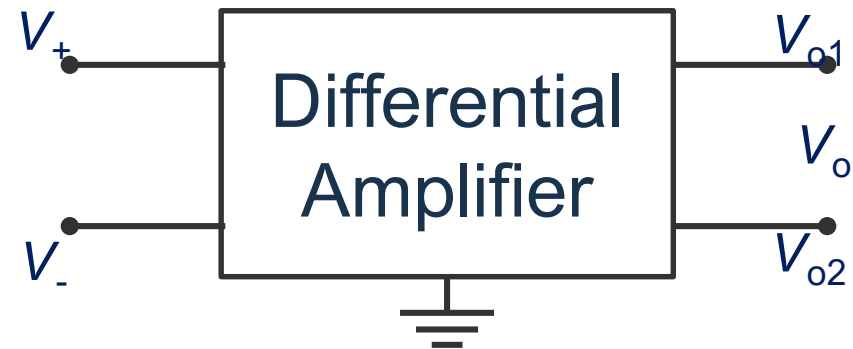

# Important Features an OpAmp

- It has Infinite Differential Voltage Gain  $A_d$


$$A_d = \frac{V_o}{V_+ - V_-} = \infty$$

$$V_+ - V_- = \frac{V_o}{A_d} \cong 0$$

$$V_+ = V_- \text{ (Virtually Short)}$$

- OpAmp has infinite Input Impedance  $R_i = \infty$

$$I_{B1} = I_{B2} \cong 0$$

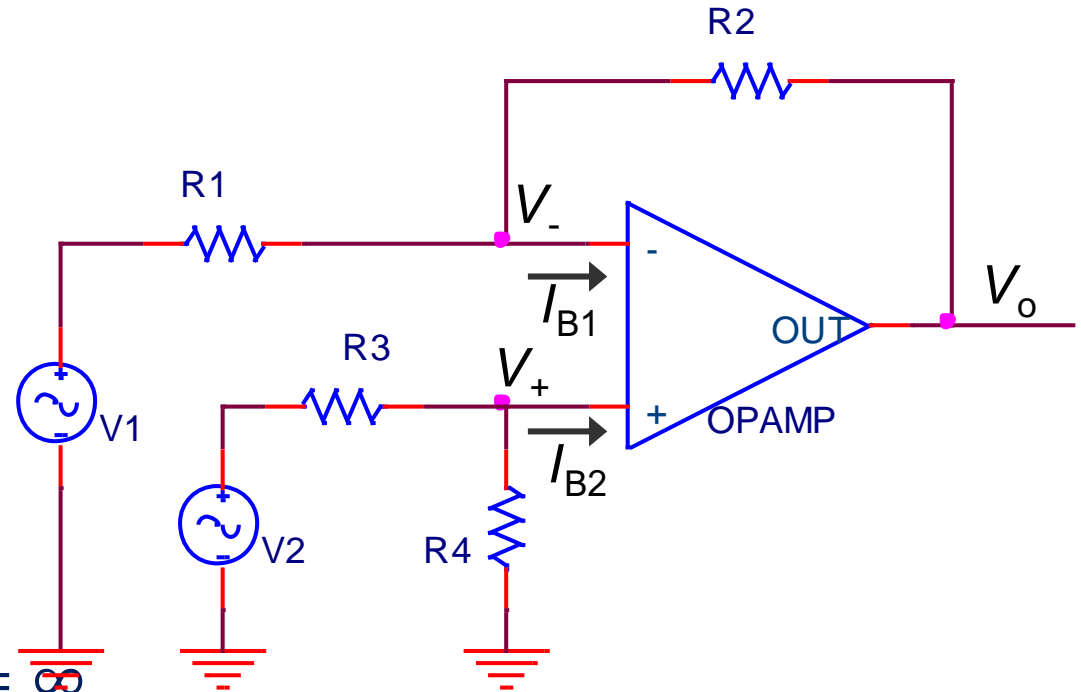

# Output Voltage due to $V_1$ only


Superposition Theorem to determine  $V_o$

**Part 1:**  $V_{o1}$  is output due to only input  $V_1$

$$V_+ \cong V_- = 0$$

$$I_1 = \frac{V_1}{R_1}$$
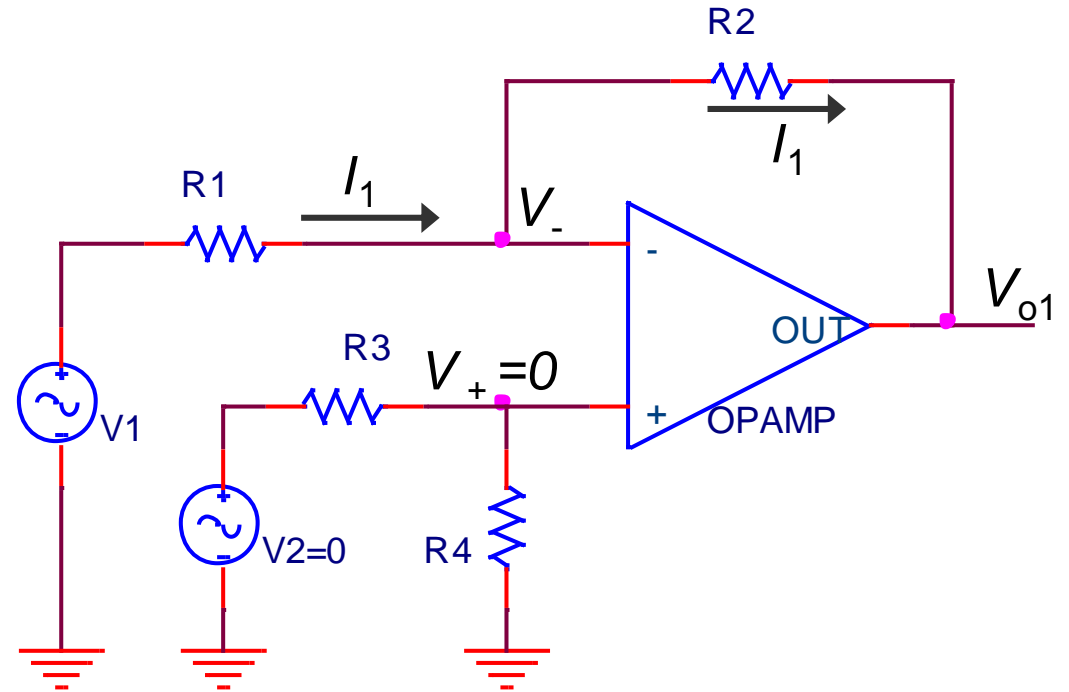
$$V_{o1} = -R_2 I_1 = -\frac{R_2 V_1}{R_1}$$



# Output Voltage due to $V_2$ only

Part2: Output is  $V_{o2}$  due to only input  $V_2$


$$V_{o2} = -I_1(R_1 + R_2) \quad (1)$$

$$V_- \cong V_+ = \frac{R_4}{R_3 + R_4} V_2$$

$$I_1 = \frac{0 - V_-}{R_1} = \frac{-R_4}{R_3 + R_4} V_2 \quad (2)$$

From (1) and (2)
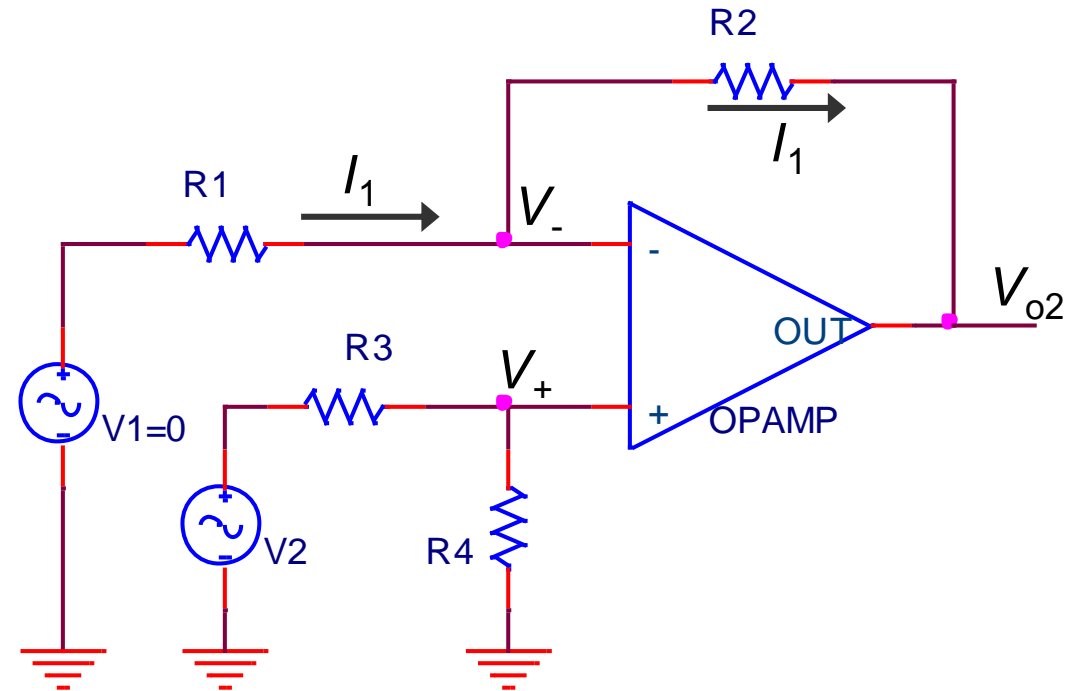
$$V_{o2} = \frac{-(R_1 + R_2)}{R_1} \frac{-R_4}{R_3 + R_4} V_2$$



# Total Output Voltage due to $V_{o1}$ and $V_{o2}$

From Superposition theorem Output Voltage

$$V_o = V_{o1} + V_{o2}$$

$$V_o = -\frac{R_2}{R_1} V_1 + \frac{R_1 + R_2}{R_1} \frac{R_4}{R_3 + R_4} V_2$$

Assume,  $R_1 = R_3$  and  $R_2 = R_4$

$$V_o = \frac{R_1 + R_2}{R_1} \frac{R_2}{R_1 + R_2} V_2 - \frac{R_2}{R_1} V_1$$

$$V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

