

<http://DrSatvir.in>

---

# LINEAR INTEGRATED CIRCUITS

## PART-03

### DC Analysis of BJT Differential Amplifier Circuit

**DR SATVIR SINGH**

DEPARTMENT OF ECE

IKG PUNJAB TECHNICAL UNIVERSITY

KAPURTHALA - 144603 (PB) INDIA


Do Like, Share & Subscribe

---

# DC Analysis

It involves determination of operating-point current  $I_{CQ}$  and voltage  $V_{CEQ}$ . This analysis remains same for all types of BJT Differential Amplifiers, whether it is a

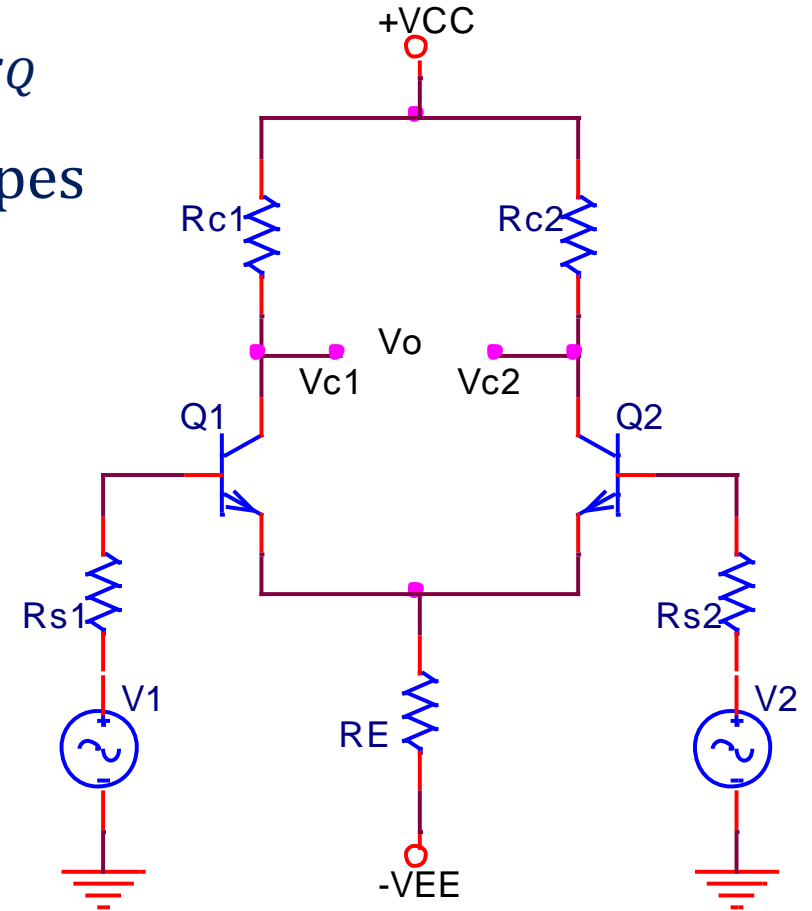
1. Dual Input Balanced Output
2. Dual Input Unbalanced Output
3. Single-Input Balanced Output
4. Single-Input Unbalanced Output



# DC Analysis of Differential Amplifier

Important consideration for DC Analysis

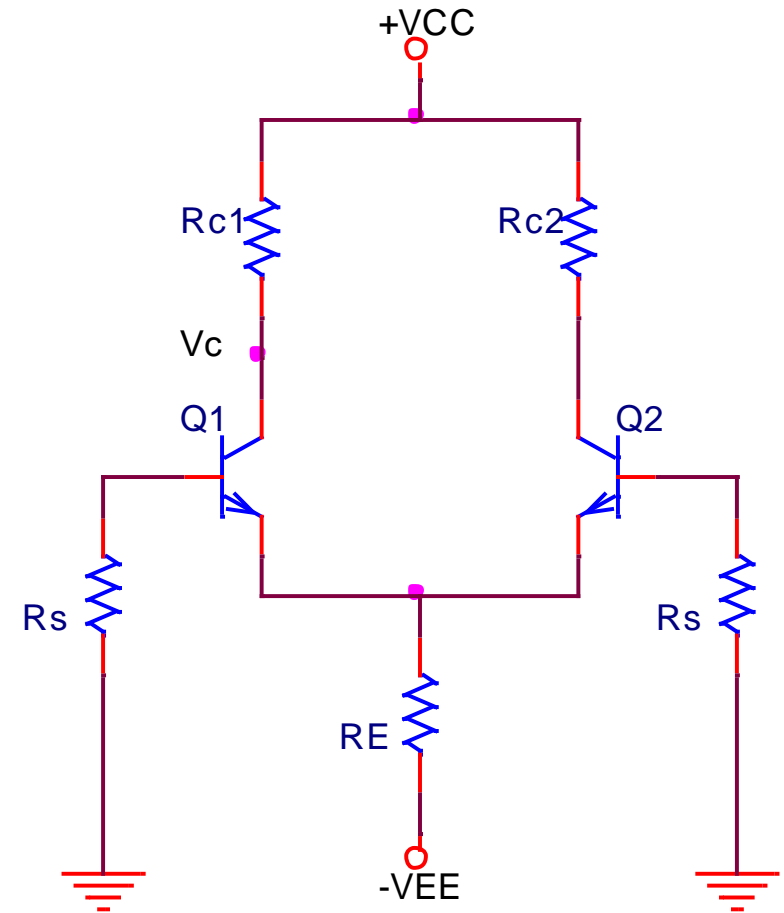1. Identical BJTs  $Q_1$  &  $Q_2$  are connected in symmetry
2. Hence, they will have same  $I_{CQ}$  and  $V_{CEQ}$
3. Amplifier has two DC supplies;  $+V_{CC}$  and  $-V_{EE}$
4. Reduce input AC signals to zero;  $V_1 = V_2 = 0$ .
5. Source resistances are same;  $R_{S1} = R_{S2} = R_S$



# Determination of $I_C$

To determine  $I_C$  apply let's use KVL

$$R_S I_B + V_{BE} + 2I_E R_E = V_{EE} \quad (1)$$

We know that  $I_B = (I_C \cong I_E)/\beta$ . Let's put  $I_B$  in (1)


$$R_S I_E / \beta + V_{BE} + 2I_E R_E = V_{EE}$$

$$(R_S / \beta + 2R_E) I_E = V_{EE} - V_{BE}$$

$$I_E = \frac{V_{EE} - V_{BE}}{(R_S / \beta + 2R_E)} \cong I_C$$

Further  $R_S / \beta \ll 2R_E$
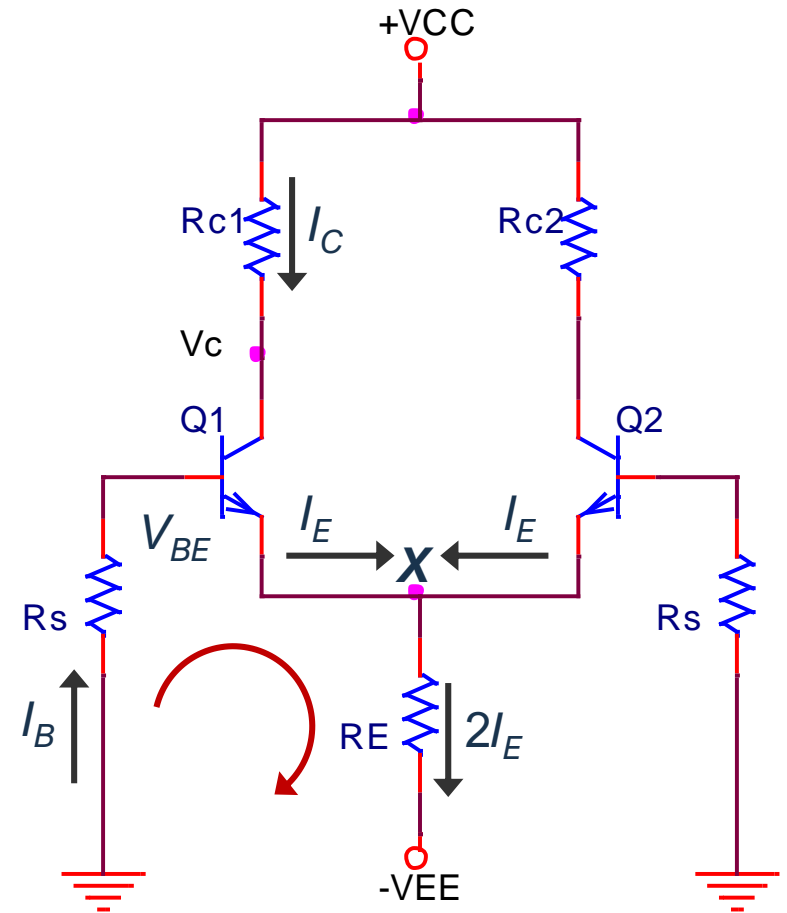
$$I_C = I_E = \frac{V_{EE} - V_{BE}}{2R_E}$$



# Determination of $V_{CEQ}$

$V_{CE}$  is given as

$$V_{CE} = V_C - V_E \quad (2)$$


If we assume  $R_{C1} = R_{C2} = R_C$ , using KVL collector terminal voltage

$$V_C = V_{CC} - I_C R_C$$

Further,  $V_{BE} = V_B - V_E$  but  $V_B = -I_B R_S \cong 0$  that leads to  $V_E \cong -V_{BE}$ . Substitute  $V_C$  and  $V_E$  in (2)

$$V_{CE} = (V_{CC} - I_C R_C) - (-V_{BE})$$

$$V_{CE} = V_{CC} + V_{BE} - I_C R_C$$

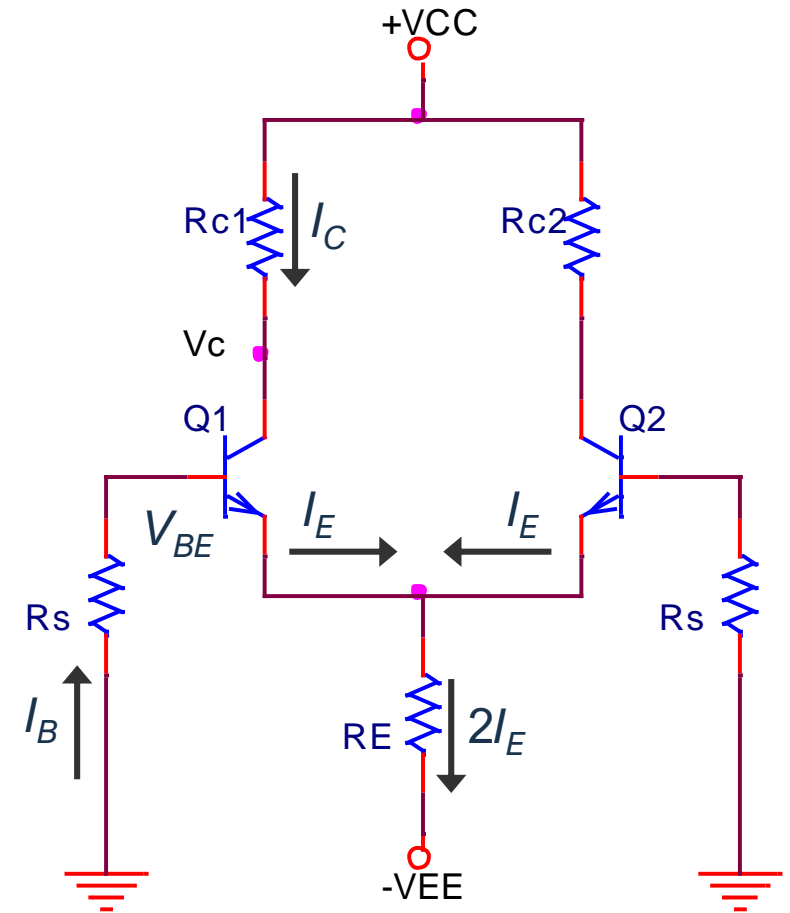

# Numerical Problem


Determine operating points current and voltage when  $R_{S1} = R_{S2} = 50\Omega$ ,  $R_E = 4.7k\Omega$  and  $R_C = 2.2k\Omega$ . Transistors are biased using  $\pm 10V$  voltage supplies. Assume DC current gain  $\beta = 100$ .

Operating point Collector current  $I_C$  is given by

$$I_C = \frac{V_{EE} - V_{BE}}{(R_S/\beta + 2R_E)}$$

$$I_C = \frac{10 - 0.7}{(50/100 + 2 * 4.7k)} = \frac{9.3}{0.5 + 9400}$$

$$I_C = 0.989mA$$

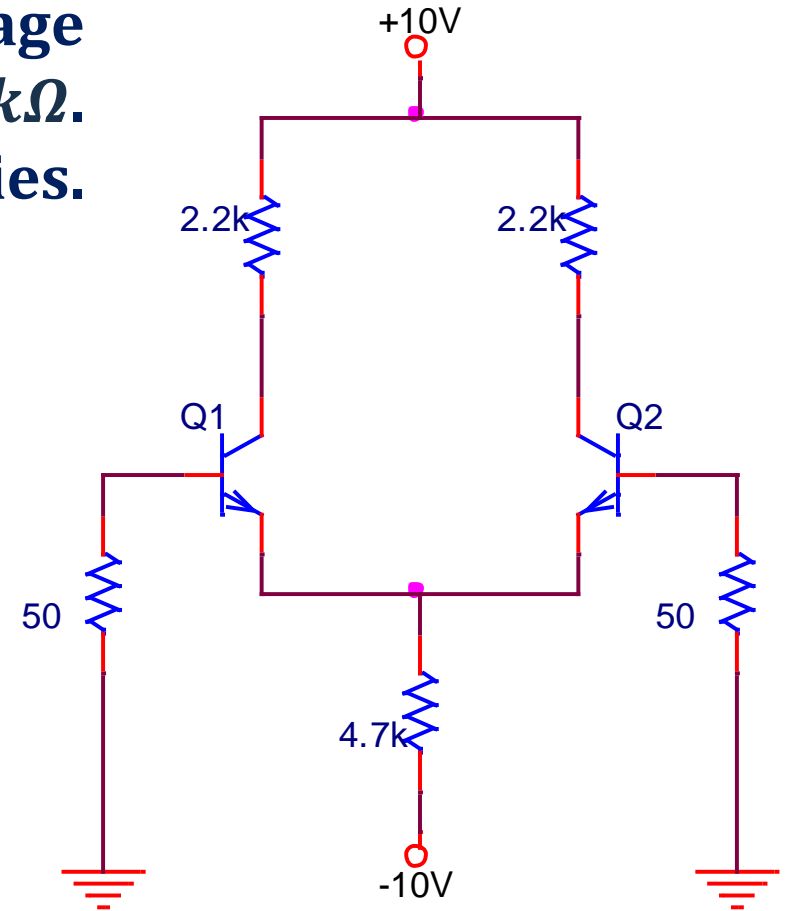

# Numerical Problem

Whereas operating point voltage  $V_{CEQ}$  is given as

$$V_{CEQ} = V_{CC} + V_{BE} - I_C R_C$$

$$V_{CEQ} = 10 + 0.7 - 0.989\text{m} * 2.2\text{k}$$

$$V_{CEQ} = 10 + 0.7 - 2.18$$

$$V_{CEQ} = 8.52\text{V}$$

