

LINEAR INTEGRATED CIRCUITS

PART-05

Advantages of Swamping Resistors in Differential Amplifier

D R S A T V I R S I N G H
DEPARTMENT OF ECE
IKG PUNJAB TECHNICAL UNIVERSITY
KAPURTHALA - 144603 (PB) INDIA

Do Like, Share & Subscribe

Differential Amplifier

- Differential Voltage Gain

$$A_d = \frac{R_C}{r_e}$$

- Input Resistance


$$R_i = 2\beta r_e$$

- Further, Dynamic Emitter Resistance r_e is

$$r_e = \frac{\eta V_T}{I_E}$$

$V_T = kT \approx 25mV$ at room temperature

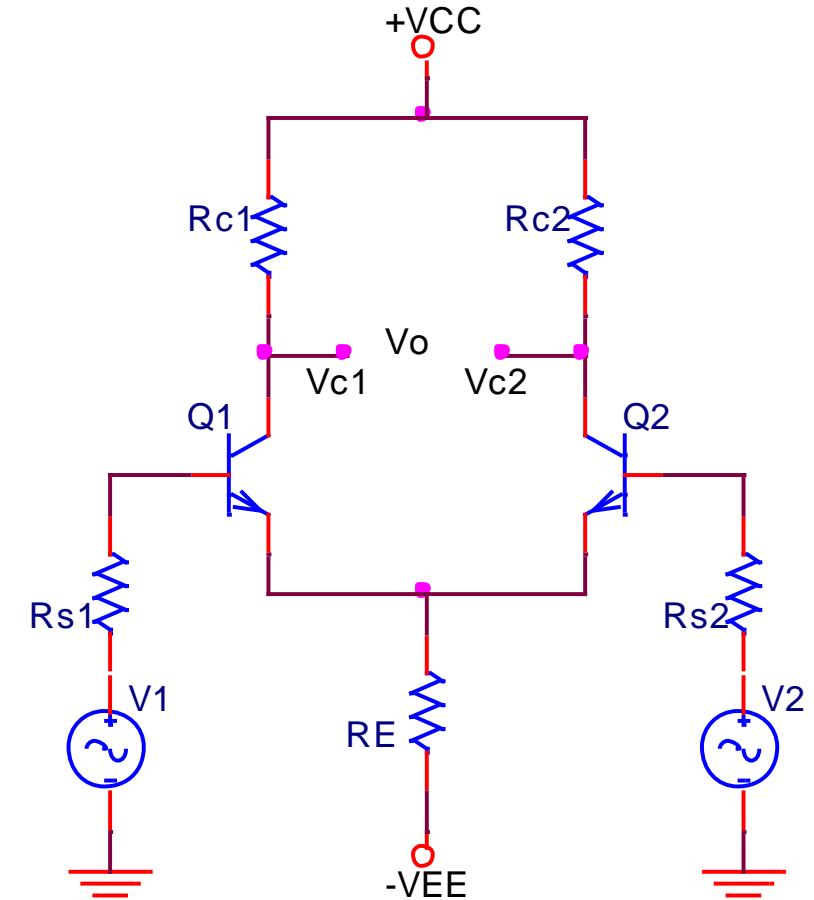- Consequently, A_d and R_i depend upon temperature



Refer: Part-04 AC Analysis of
BJT Differential Amplifiers

Effect of Swamping Resistance

To reduce the effect of temperature (r_e), an external resistance R'_E is placed in series with emitter terminal

DC Analysis ($V_1 = V_2 = 0$)

KVL in input loop


$$I_B R_s + V_{BE} + I_E R'_E + 2I_E R_E = V_{EE}$$

Replace $I_B = I_E / \beta$

$$R_s I_E / \beta + I_E R'_E + 2I_E R_E = V_{EE} - V_{BE}$$

Simplification gives
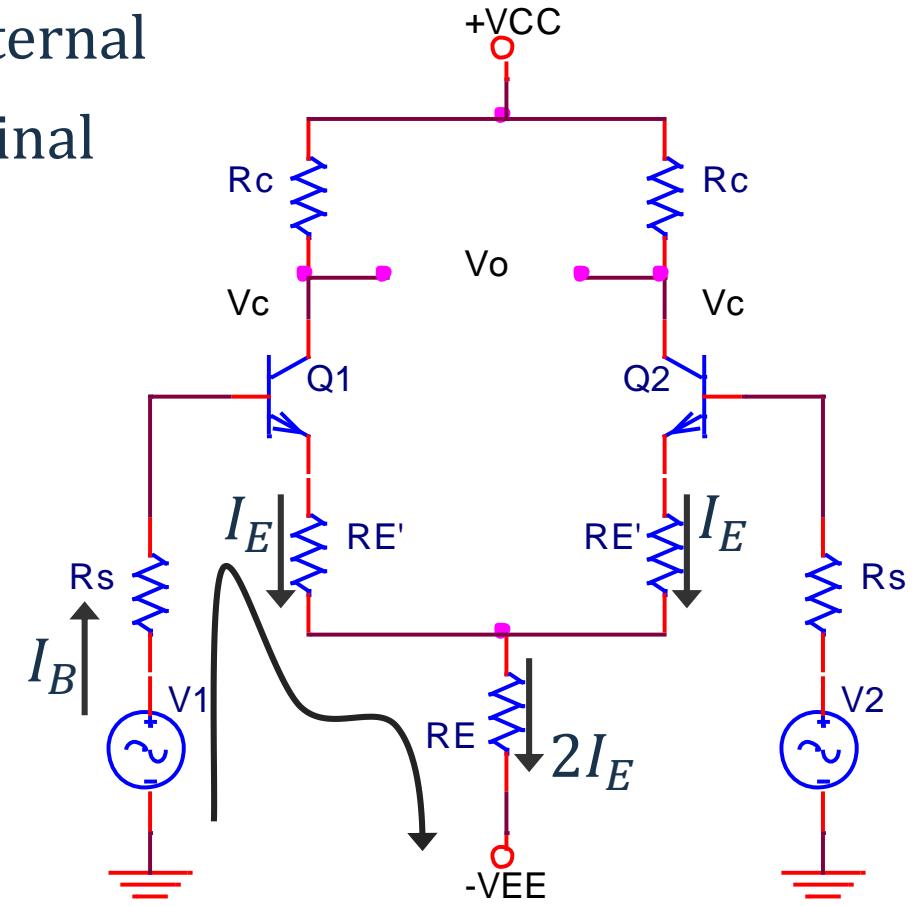
$$I_E = \frac{V_{EE} - V_{BE}}{R'_E + 2R_E + R_s / \beta} \approx \frac{V_{EE} - V_{BE}}{R'_E + 2R_E} \approx I_C$$



Refer: Part-03 DC Analysis of
BJT Differential Amplifiers

Effect of Swamping Resistance

Collector to Emitter voltage is given as

$$V_{CE} = V_C - V_E \quad (1)$$

$$V_C = V_{CC} - I_C R_C$$


Further, $V_{BE} = V_B - V_E$ but $V_B = -I_B R_S \approx 0$

$$V_E \approx -V_{BE}$$

Substitute V_C and V_E in (1)

$$V_{CE} = (V_{CC} - I_C R_C) - (-V_{BE})$$

$$V_{CE} = V_{CC} - I_C R_C + V_{BE}$$

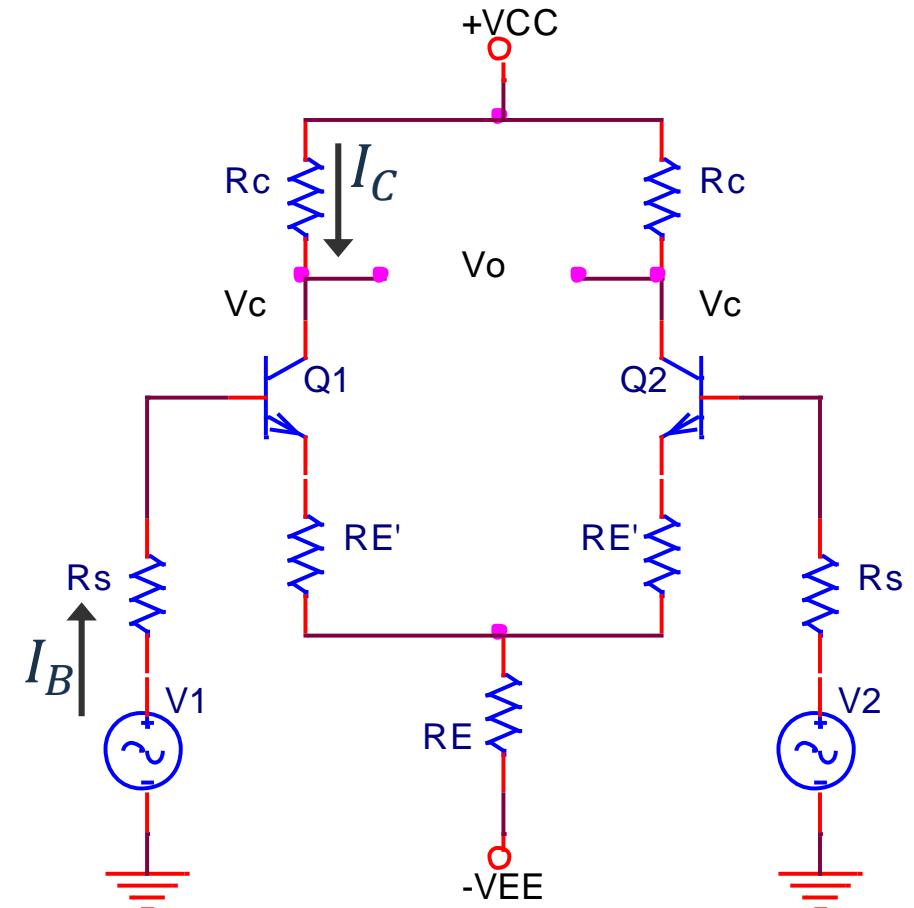

Refer: Part-03 DC Analysis of
BJT Differential Amplifiers

Effect of Swamping Resistance

AC analysis ($V_{CC} = V_{EE} = 0$)


Differential Voltage Gain is given

$$A_d = \frac{R_C}{r_e + R'_E} \approx \frac{R_C}{R'_E}$$

Similarly Input Resistance is given as

$$R_{i1} = R_{i2} \approx 2\beta(r_e + R'_E) \approx 2\beta R'_E$$

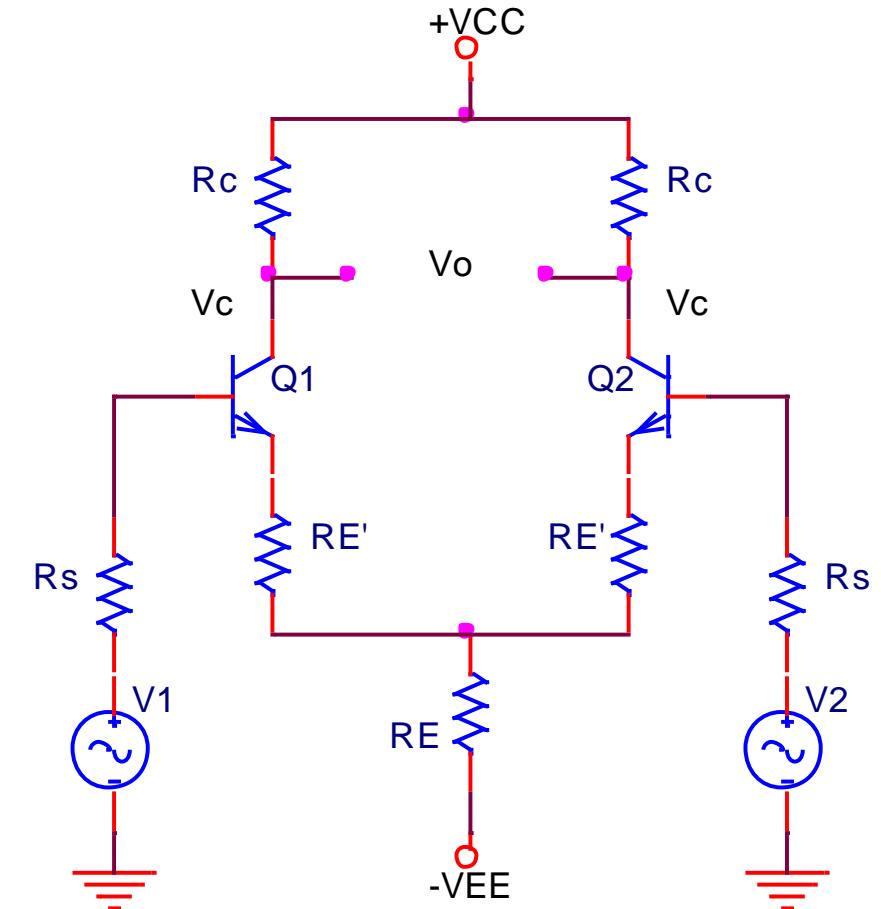Hence, Swamping Resistance R'_E reduces the dependency of Voltage Gain and Input Resistances on r_e (temperature as well).




Refer: Part-04 AC Analysis of
BJT Differential Amplifiers

Numerical Problem – Statement

Let's consider a Dual Input Balanced Output Differential circuit having $R_C = 2.2\text{k}\Omega$, $R_E = 4.7\text{k}\Omega$, $R_S = 50\Omega$, $V_{CC} = +10V$, $V_{EE} = -10V$, $\beta = 100$ and $V_{BE} = 0.7V$. Here Swamping Resistance is $R'_E = 1\text{k}\Omega$ ($r_e \approx 25.3\Omega$).

Determine

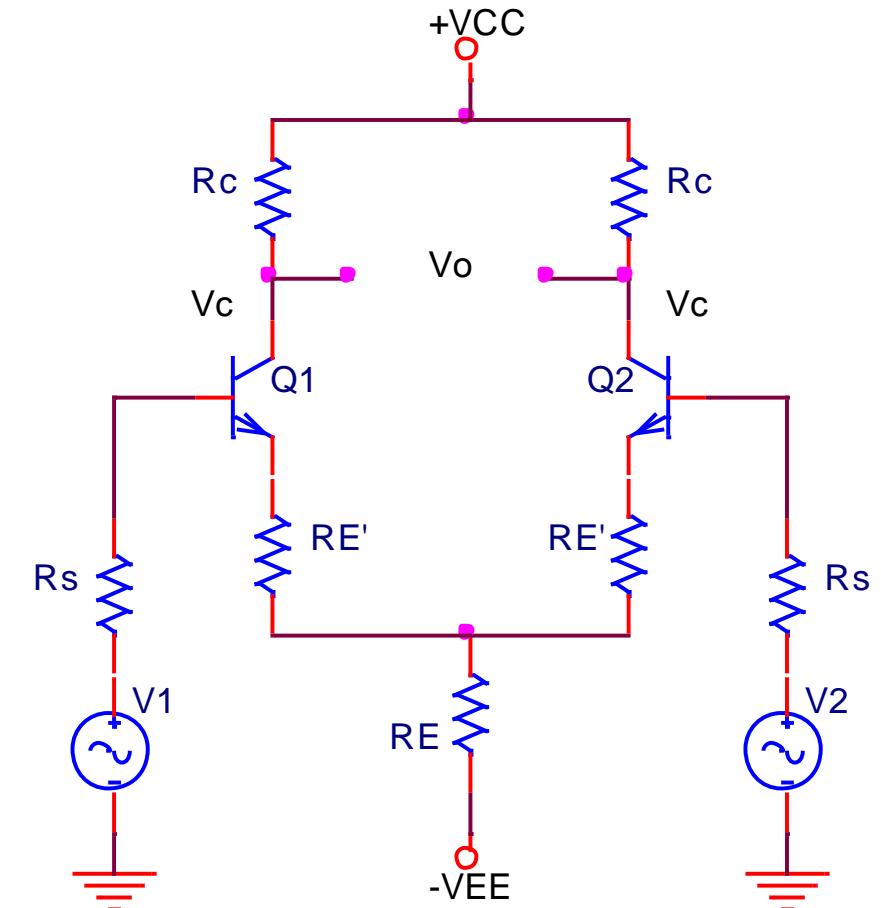- (1) Q-point I_{CQ} & V_{CEQ}
- (2) Differential Voltage Gain A_d
- (3) Input Resistances R_i
- (4) Output Resistance R_o



Numerical Problem – Solution

(1) Operating Point Current is given as

$$I_{CEQ} = \frac{V_{EE} - V_{BE}}{R'_E + 2R_E + R_s/\beta}$$


$$I_{CEQ} = \frac{10 - 0.7}{1k + 2 * 4.7k + 50/100} = \frac{9.3}{1k + 9.4k + 0.5}$$

$$I_{CEQ} = 0.894mA$$

Operating Point Voltage is give by

$$V_{CEQ} = V_{CC} - I_C R_C + V_{BE}$$
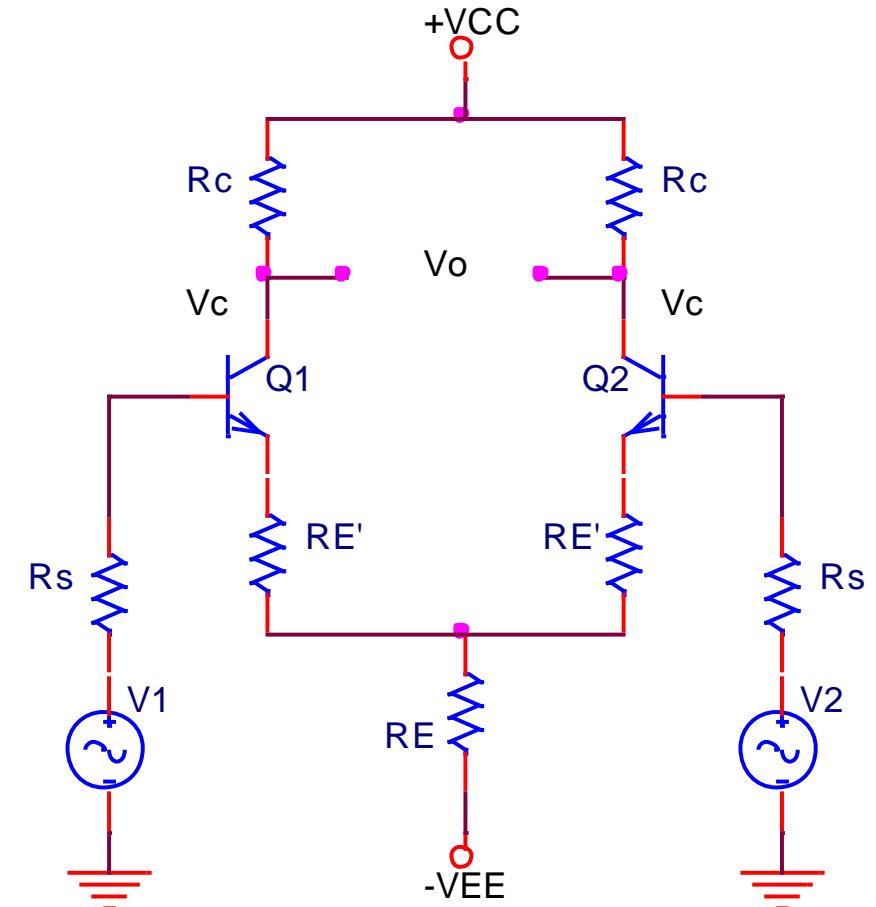
$$V_{CEQ} = 10 - 0.894m * 2.2k + 0.7 = 7.33V$$



Numerical Problem – Solution

(2) Differential Voltage Gain is given

$$A_d = \frac{R_C}{R'_E}$$


$$A_d = \frac{2.2k}{1k} = 2.2$$

(3) Input resistances are

$$R_i = 2\beta R'_E = 2 * 100 * 1k = 200k\Omega$$

(4) Output resistances are

$$R_o = R_C = 2.2k\Omega$$

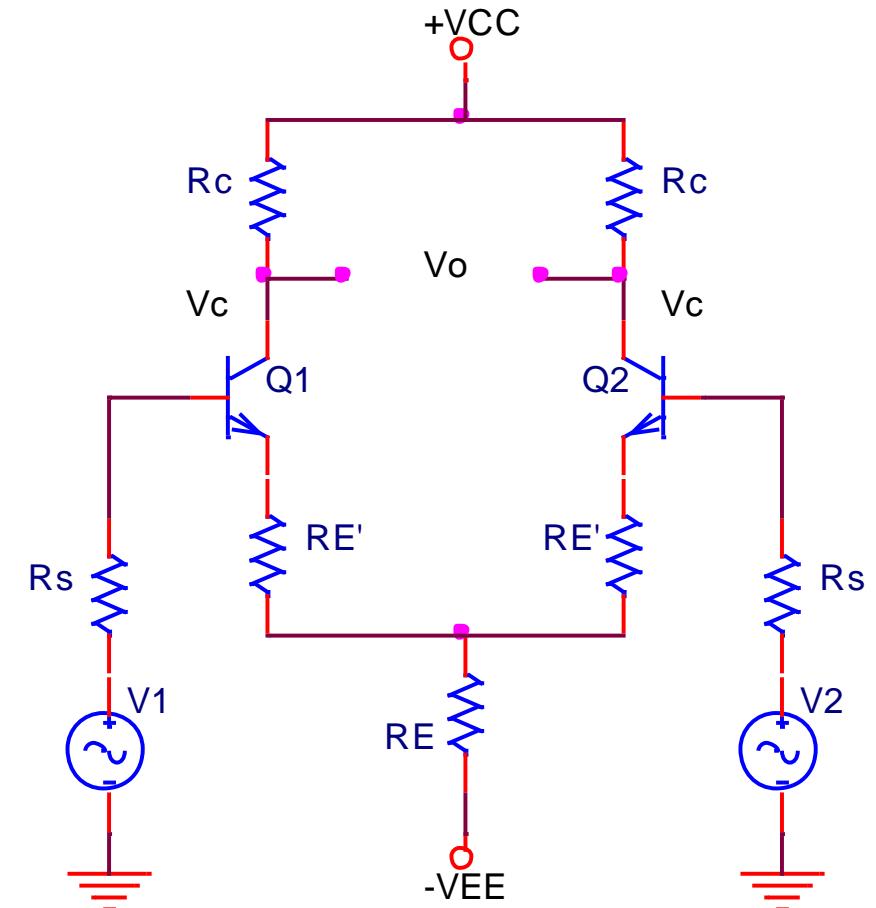

<http://DrSatvir.in>

LINEAR INTEGRATED CIRCUITS

Thank You

DR SATVIR SINGH
DEPARTMENT OF ECE
IKG PUNJAB TECHNICAL UNIVERSITY
KAPURTHALA - 144603 (PB) INDIA

Do Like, Share & Subscribe