

LINEAR INTEGRATED CIRCUITS

Ideal Op-Amp,
Practical OpAmp,
Equivalent Circuit &
Transfer Curves of OpAmps

DR SATVIR SINGH

Ph.D., M.E., B.Tech., FIE, FIETE

IKGPTU Main Campus Kapurthala (PB) India

Subscribe for more videos. <http://DrSatvir.in>

Ideal OpAmp Parameters

Open Loop Voltage Gain

$$A_d = \frac{V_o}{V_{id}} = \frac{V_o}{V_+ - V_-} = \infty$$


Input Resistance $R_i = \infty$

Output Resistance $R_o = 0$

Bandwidth $BW = \infty$


Input Offset Voltage $V_{io} = 0$

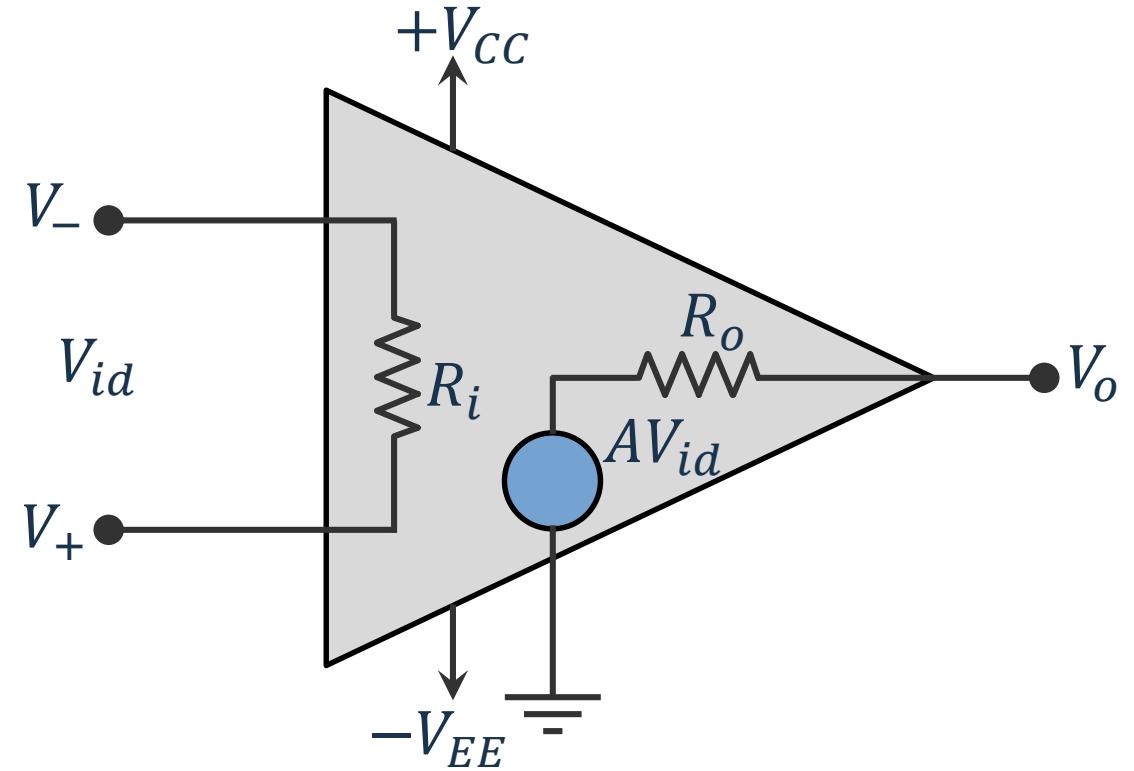Common Mode Rejection Ratio $CMRR = \infty$



Ideal Vs Practical OpAmp IC741

S. No.	Parameters	Ideal	Practical
1.	Open Loop Voltage Gain $A_d = \frac{V_o}{V_+ - V_-}$	∞	100dB
2.	Input Resistance R_i	∞	2MΩ
3.	Output Resistance R_o	0	75Ω
4.	Bandwidth BW	∞	1MHz
5.	Input Offset Voltage V_{io}	0	6mV
6.	Input Offset Current $I_{io} = I_{B1} - I_{B2}$	0	200nA
7.	Input Bias Current $I_B = \frac{I_{B1} + I_{B2}}{2}$	0	500nA
8.	Slew Rate $\frac{dV_o}{dt}$	∞	0.5V/ μ Sec
9.	CMRR $\frac{A_d}{A_{cm}}$	∞	80dB
10.	PSRR or SVRR $\frac{\Delta V_{io}}{\Delta V}$	0	150 μ V/V

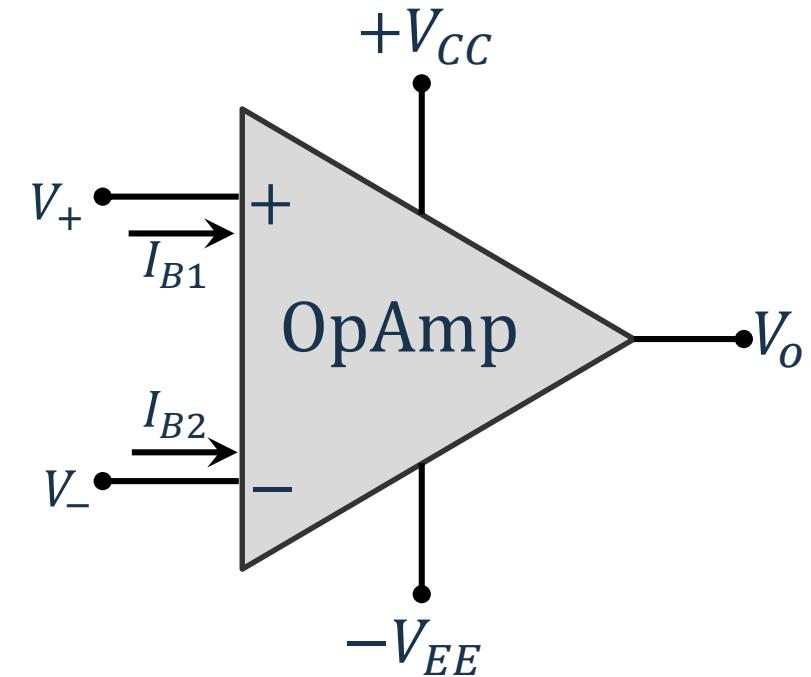

Equivalent Circuit Diagram

Differential Input Voltage


$$V_{id} = V_+ - V_-$$

$$\text{Voltage Gain, } A = \frac{V_o}{V_{id}} \approx \infty$$



$$V_{id} = \frac{V_o}{A} = 0 \Leftrightarrow V_+ = V_-$$

This is call **Virtual Short Circuit**

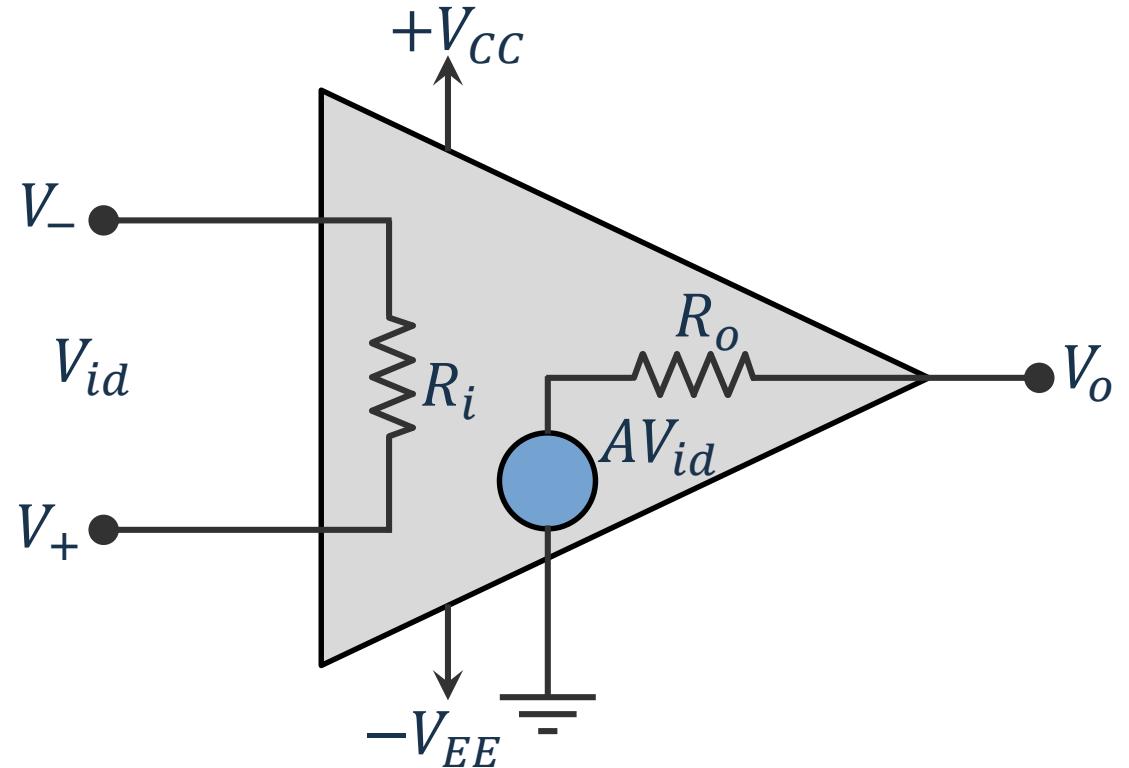Ideally, $R_o = 0\Omega$ and $R_i = \infty$



Transfer Curve

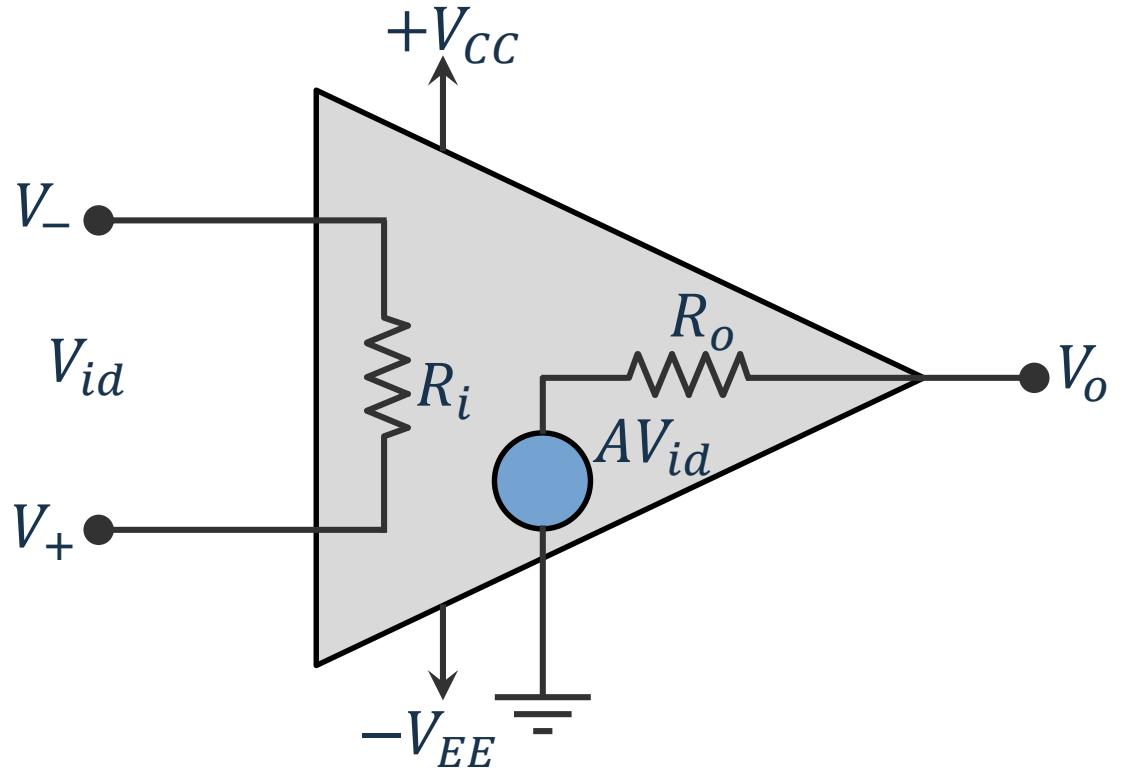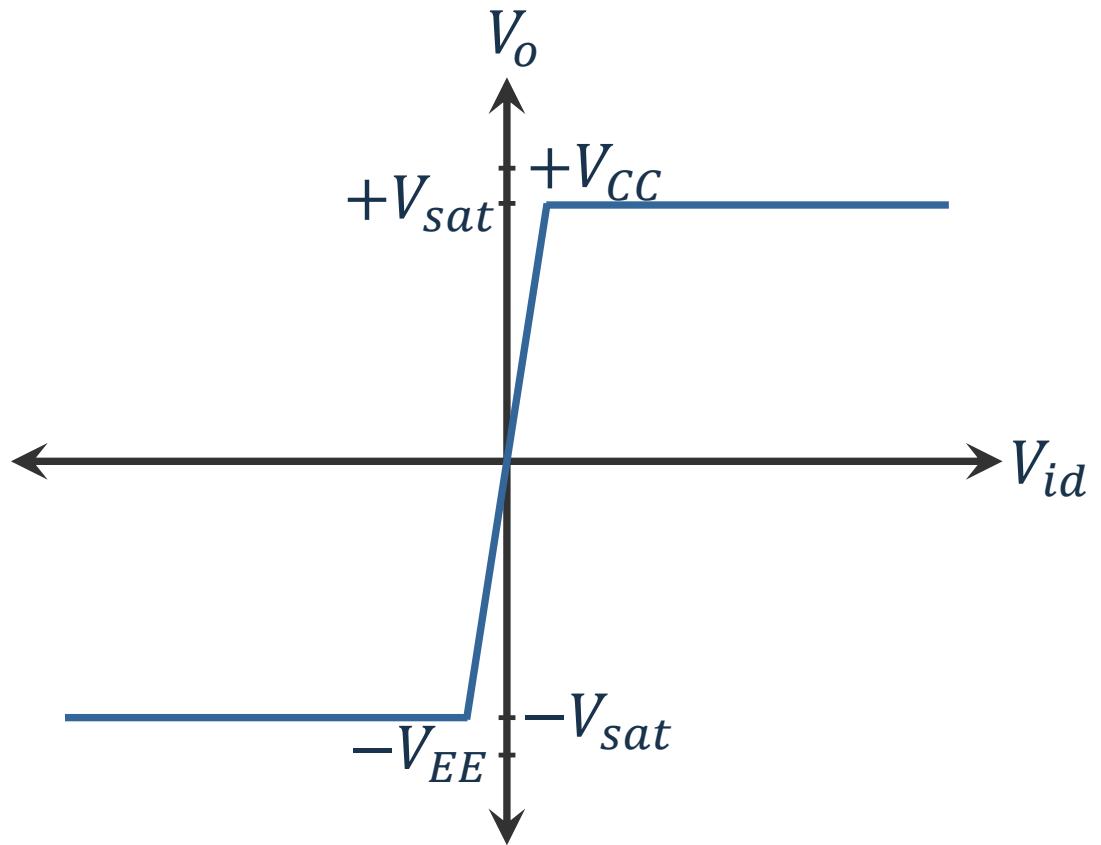

LINEAR INTEGRATED CIRCUITS

THANK YOU

DR SATVIR SINGH

Ph.D., M.E., B.Tech., FIE, FIETE

IKGPTU Main Campus Kapurthala (PB) India

Subscribe for more videos. <http://DrSatvir.in>