


**Dr Satvir Singh**

---

# **LINEAR INTEGRATED CIRCUITS**

**3-02**

**Instrumentation Amplifier**

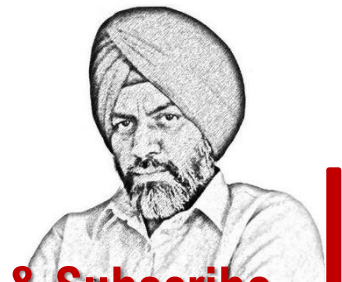

**Do Like, Share & Subscribe**

---

<http://DrSatvir.in>

# Instrumentation Amplifier

---

Most of home & industrial appliances involve measurements of physical parameters for auto-control of processes. Such instruments use transducers to convert physical quantities into electrical signals, which usually need to be amplified.


For example, a strain gauge undergoes a change in **resistance** (an electrical parameter) when subjected to **pressure** (a physical parameter). Corresponding voltage signals are very small that need to be amplified.

Many a times amplifications are also required to activate next stages of processes.

Op-Amp based differential amplifier is preferred amplifier to amplify very weak signals due to its high gain and capability of suppression of ambient noise.

# Block Diagram

---

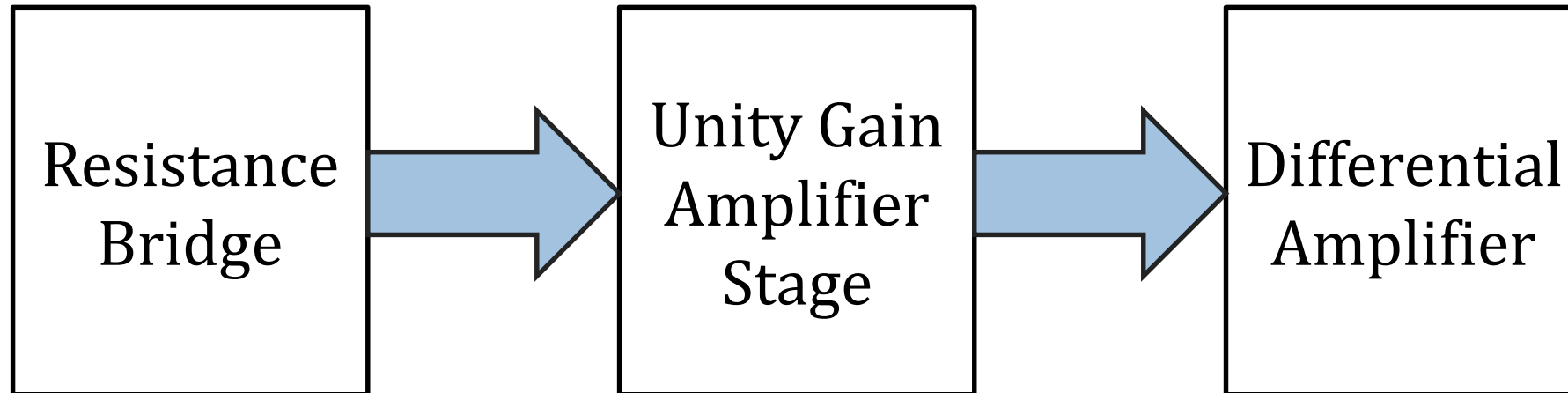

# Instrumentation Amplifier

$R_T$  is the transducer resistance under normal conditions. It observes change  $\Delta R$  when subjected to physical changes.

Under unbalance condition


$$V_d = V_A - V_B \neq 0$$

$$V_d = \frac{(R_T + \Delta R)V_{DC}}{R_T + \Delta R + R_C} - \frac{R_B V_{DC}}{R_A + R_B}$$

For simplicity, assume

$$R_A = R_B = R_C = R_T = R$$
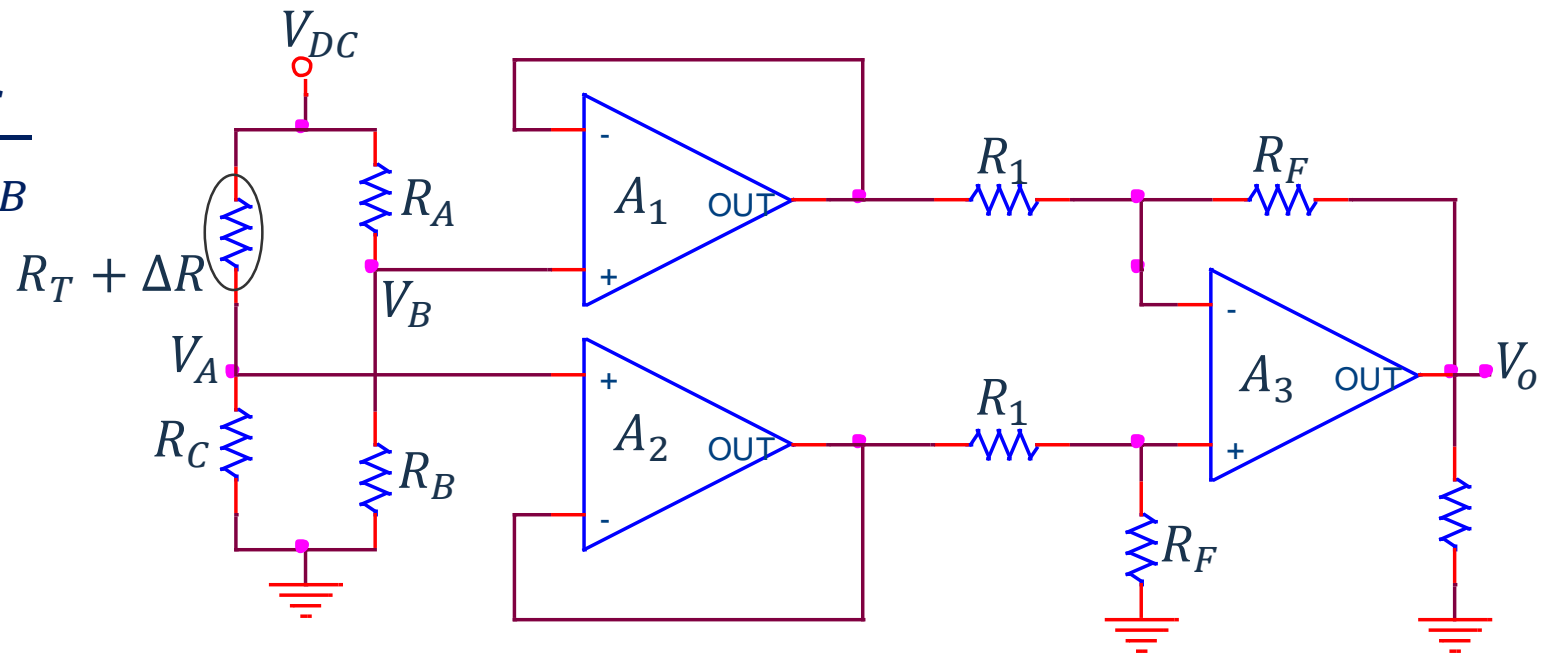
$$V_d = \frac{\Delta R V_{DC}}{2(2R + \Delta R)}$$



# Instrumentation Amplifier


$A_1$  and  $A_2$  are unity gain non-inverting amplifiers with high input impedance and draw negligible current from transducer, hence provide isolation.

Next stage is differential amplifier  $A_3$  that suppresses common noise and amplifies the difference between both inputs.

$$V_o = \frac{R_F}{R_1} \frac{\Delta R V_{DC}}{2(2R + \Delta R)}$$

Since,  $2R + \Delta R \approx 2R$ , Output of Instrumentation Amplifier is
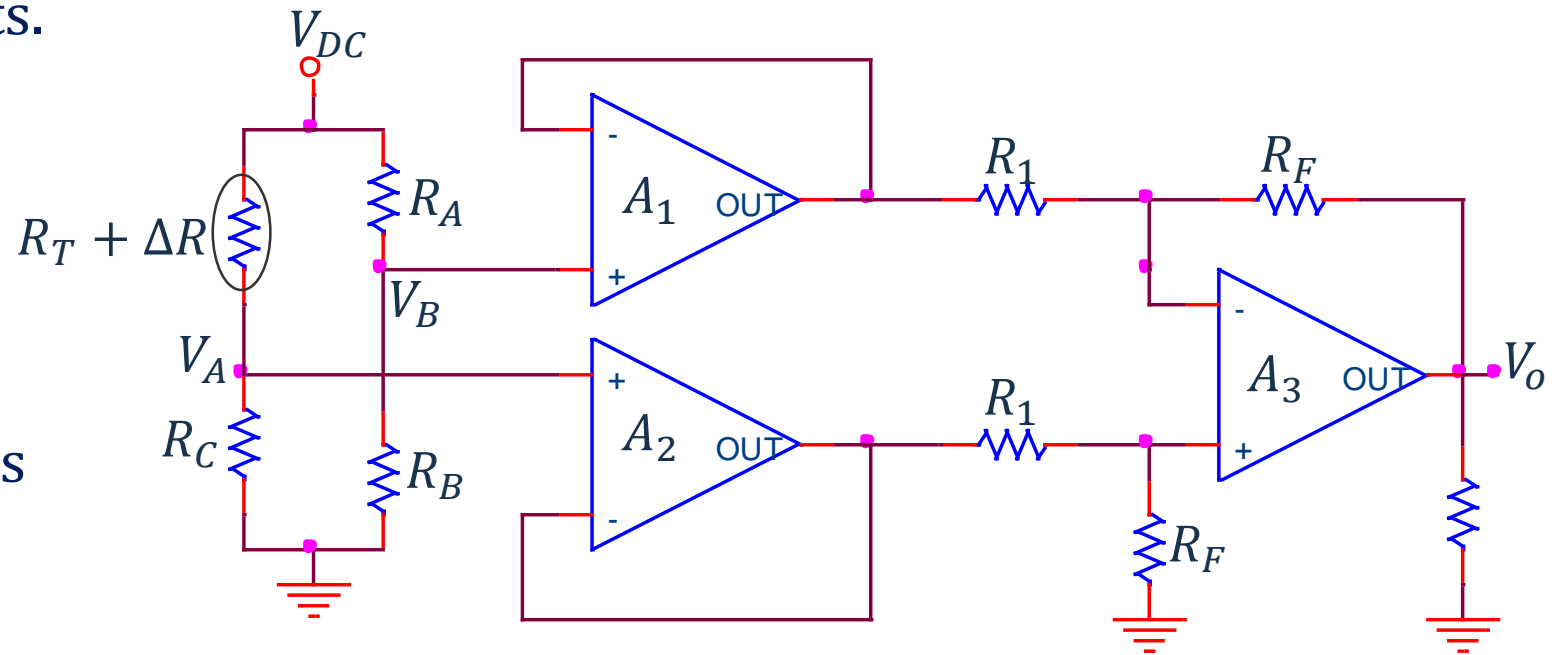
$$V_o = \frac{\Delta R}{4R} \frac{R_F}{R_1} V_{DC}$$



**Dr Satvir Singh**

---

# **LINEAR INTEGRATED CIRCUITS**

**Thank You**

**Do Like, Share & Subscribe**

---

*<http://DrSatvir.in>*