

# **LINEAR INTEGRATED CIRCUITS**

**3-08**

**Butterworth LPF, HPF & Higher Order Filters**

**Do Like, Share & Subscribe**

---

# Outline

---

1. Active Filters
2. Butterworth Active Filters
3. First Order Low Pass Filter
4. Second Order Low Pass Filter
5. First Order High Pass Filter
6. Second Order High Pass Filter
7. Higher Order Filters

# Filter Classification

---

## **Analog & Digital Filters**

Digital filters use digital techniques to filter analog signals.

Analog filters are meant to filter analog signals. These can be, further, classified as Active and Passive Filters.

## **Passive & Active Filters**

Passive filters use linear components, i.e., Resistors, Capacitors and Inductors.

Filters that uses Op-Amp & Transistors, etc. semiconductor components in addition to Resistors & Capacitor. Inductors are not used in filters due to their large size, cost and magnetic interference.

# Advantages of Active Filters

---

## **Gain & Frequency Adjustment**

In active filters, Op-Amp provides voltage gain in pass band rather than attenuation like passive filters.





## **No Loading Problem**

Op-Amp offers high input impedance and low output impedance. Therefore, active filter do not pose loading problem of the source and load.

## **Cost**

Active filters do not use inductors, therefore, are cost effective than passive filters.

# Frequency Response of Filters

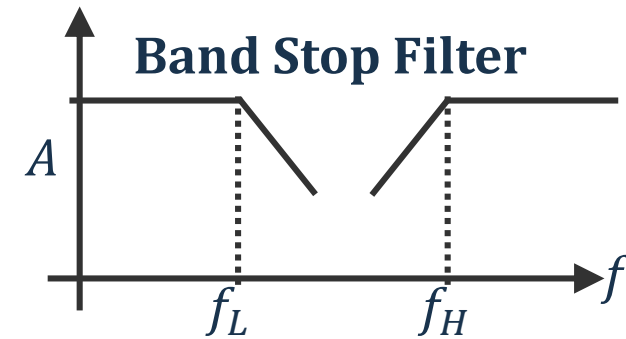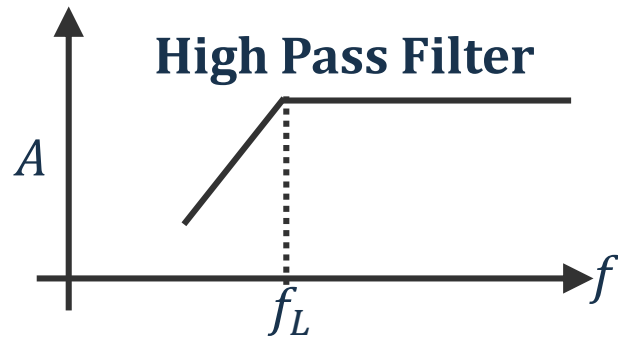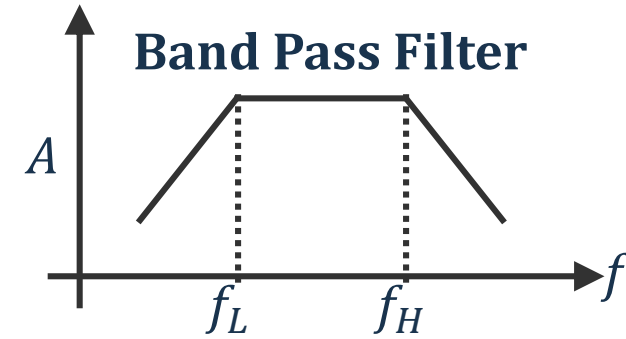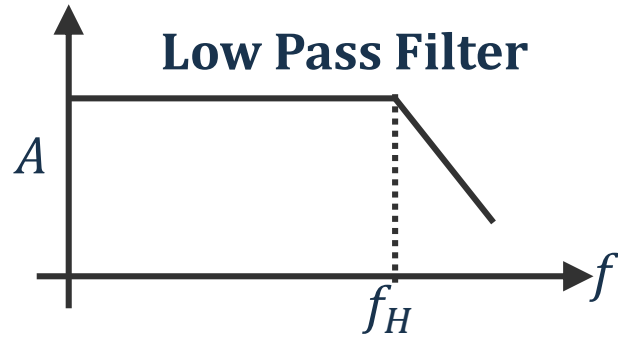

# First Order Butterworth LPF

The output of non-inverting amplifier is

$$v_o = \left(1 + \frac{R_F}{R_1}\right) v_1$$

Where  $v_1$  is voltage at the non-inverting input terminal.


This  $v_1$  voltage is given as

$$v_1 = \frac{-jX_C}{R - jX_C} v_{in}$$

Put  $-jX_C = \frac{1}{j2\pi fC}$  in above equations, and simplify

$$v_o = \left(1 + \frac{R_F}{R_1}\right) \frac{v_{in}}{1 + j2\pi fRC}$$
$$\frac{v_o}{v_{in}} = \frac{A_F}{1 + j2\pi fRC} = \frac{A_F}{1 + j\left(\frac{f}{f_H}\right)}$$

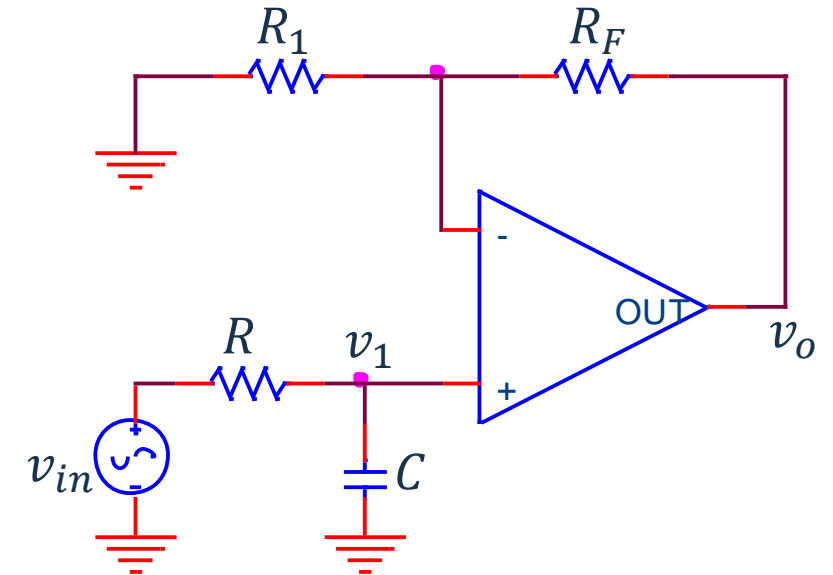Here  $A_F = 1 + \frac{R_F}{R_1}$ ,  $f$  is the input signal frequency,  $f_H = \frac{1}{2\pi RC}$  high cut-off frequency



# First Order Butterworth LPF

Magnitude and phase angle can be determined as

$$\left| \frac{v_o}{v_{in}} \right| = \frac{A_F}{\sqrt{1 + (f/f_H)^2}} \quad \text{and} \quad \phi = -\tan^{-1} \left( \frac{f}{f_H} \right)$$

At very low frequencies,  $f = 0\text{Hz}$

$$\left| \frac{v_o}{v_{in}} \right| \cong A_F$$



At frequency  $f = f_H$

$$\left| \frac{v_o}{v_{in}} \right| = \frac{A_F}{\sqrt{2}} = 0.707 A_F$$

$$\left| \frac{v_o}{v_{in}} \right| = A_F 20 \log 0.707 = 3\text{dB}$$

For frequencies  $f > f_H$

$$\left| \frac{v_o}{v_{in}} \right| < A_F$$

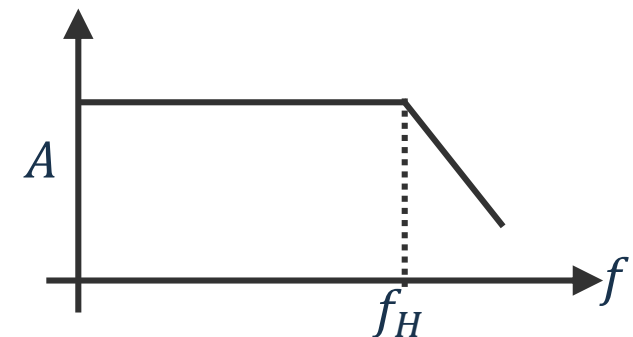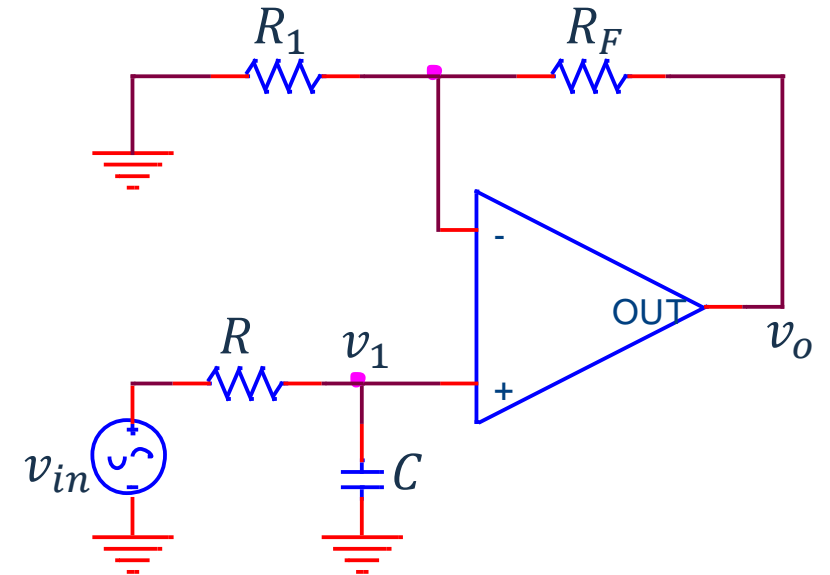

# Second Order Butterworth LPF

Applying KCL at node  $v_1$

$$I_1 = I_2 + I_3$$

$$\frac{v_{in} - v_1}{R_1} = \frac{v_1 - v_o}{1/sC_1} + \frac{v_1 - v_2}{R_2} \quad (1)$$

Using voltage divider rule

$$v_2 = \frac{1/sC_3}{R_3 + 1/sC_3} v_1 = \frac{v_1}{1 + sC_3R_3}$$



$$v_1 = (1 + sC_3R_3)v_2$$

Put in (1) and simplify

$$v_2 = \frac{R_3 v_{in} + sR_2R_3C_2 v_o}{(sR_3C_3 + 1)(R_2 + R_3 + sR_2R_3C_2) - R_2}$$

Finally the output of non-inverting amplifier
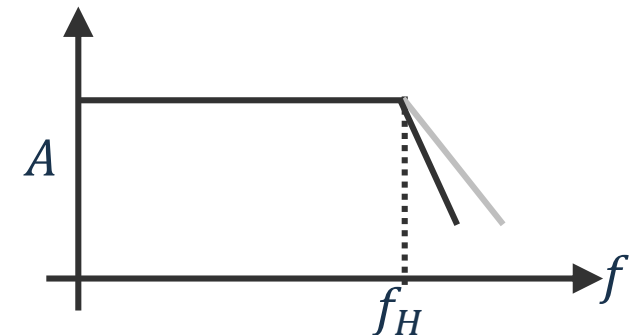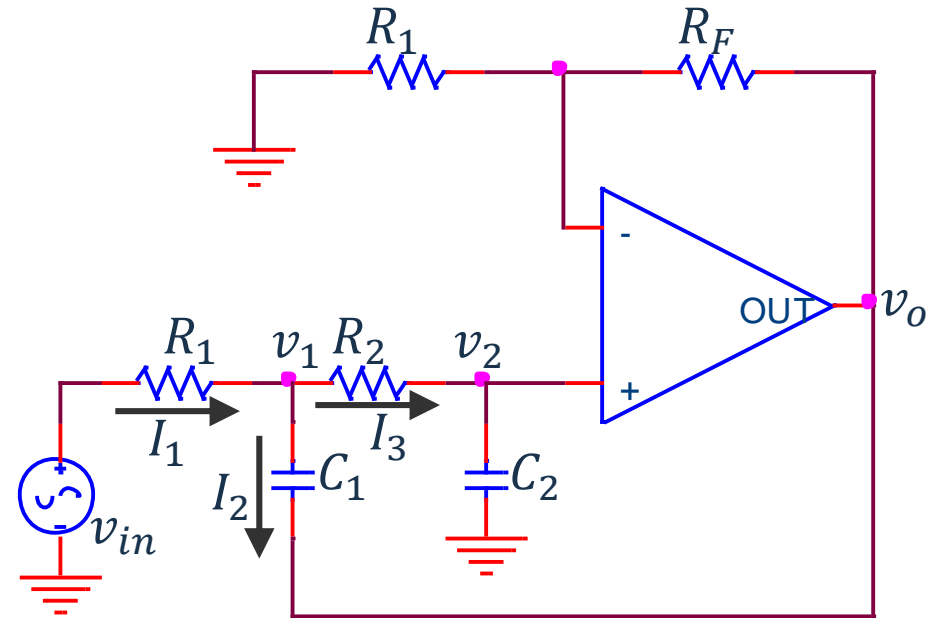
$$v_o = \left(1 + \frac{R_F}{R_1}\right) v_2 = A_F \frac{R_3 v_{in} + sR_2R_3C_2 v_o}{(sR_3C_3 + 1)(R_2 + R_3 + sR_2R_3C_2) - R_2}$$





# Second Order Butterworth LPF

Further, simply to get

$$\frac{v_o}{v_{in}} = \frac{A_F}{s^2 + \frac{s(R_3C_3 + R_2C_3 + R_2C_2 - A_FR_2C_2)}{R_2R_3C_2C_3} + \frac{1}{R_2R_3C_2C_3}}$$


For real roots of the quadratic equation in denominator, put

$$\omega_H^2 = \frac{1}{R_2R_3C_2C_3}$$

$$f_H = \frac{1}{2\pi\sqrt{R_2R_3C_2C_3}}$$

For simplicity, assume  $R_2 = R_3 = R$  and  $C_2 = C_3 = C$

$$f_H = \frac{1}{2\pi RC}$$

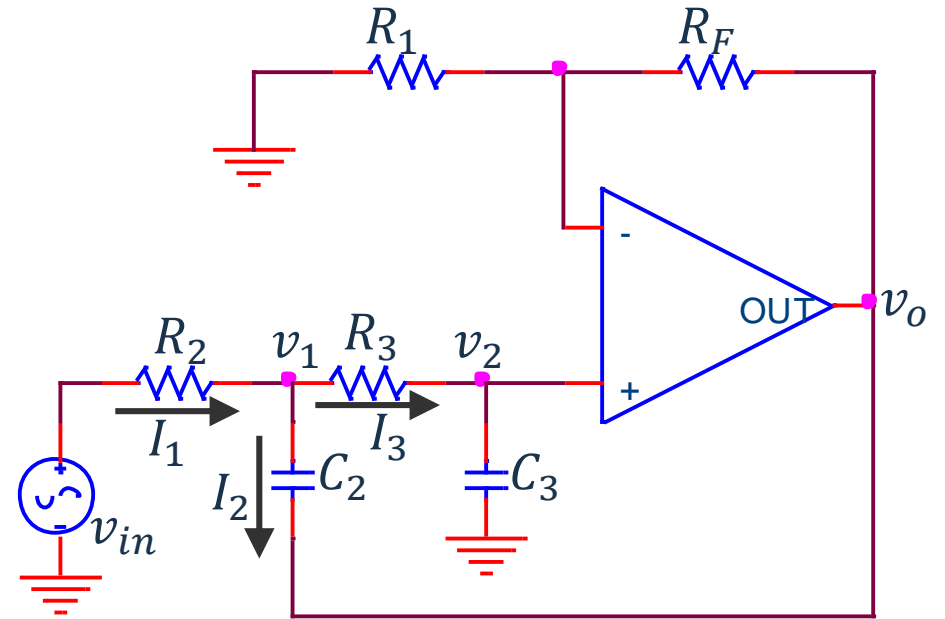

# First Order Butterworth HPF

The output of non-inverting amplifier is

$$v_o = \left(1 + \frac{R_F}{R_1}\right) v_1$$

Where  $v_1$  voltage is given as

$$v_1 = \frac{R}{R + \frac{1}{j2\pi fC}} v_{in} = \frac{j2\pi fCR}{1 + j2\pi fCR} v_{in}$$



Output of the non-inverting amplifier

$$v_o = \left(1 + \frac{R_F}{R_1}\right) \frac{j2\pi fRC}{1 + j2\pi fRC} v_{in}$$

$$\frac{v_o}{v_{in}} = A_F \frac{j2\pi fRC}{1 + j2\pi fRC} = A_F \frac{j(f/f_L)}{1 + j(f/f_L)}$$

Here,  $f_L = \frac{1}{2\pi RC}$  low cut-off frequency. Magnitude can be determined as

$$\left| \frac{v_o}{v_{in}} \right| = \frac{A_F (f/f_L)}{\sqrt{1 + (f/f_L)^2}}$$

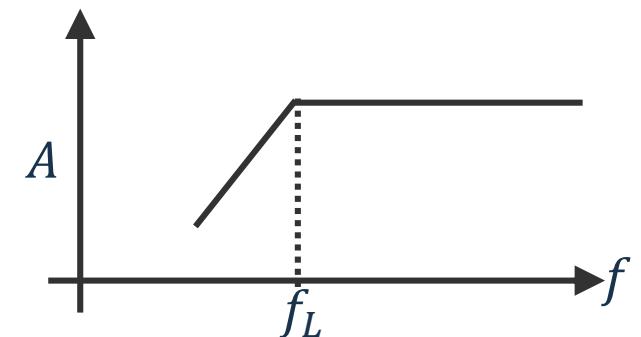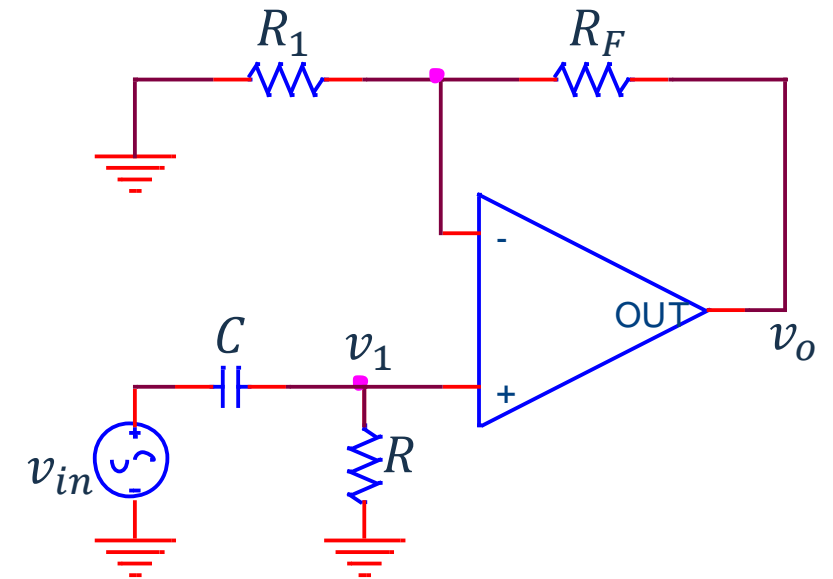



# Second Order Butterworth LPF

As we determined the cut-off frequency in Second Order Butterworth LPF, we can determine cut-off frequency of Second Order Butterworth HPF also.

$$f_L = \frac{1}{2\pi\sqrt{R_2R_3C_2C_3}}$$

For simplicity, assume  $R_2 = R_3 = R$  and  $C_2 = C_3 = C$

$$f_L = \frac{1}{2\pi RC}$$

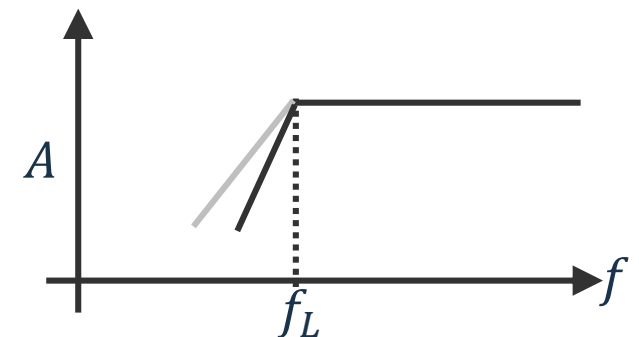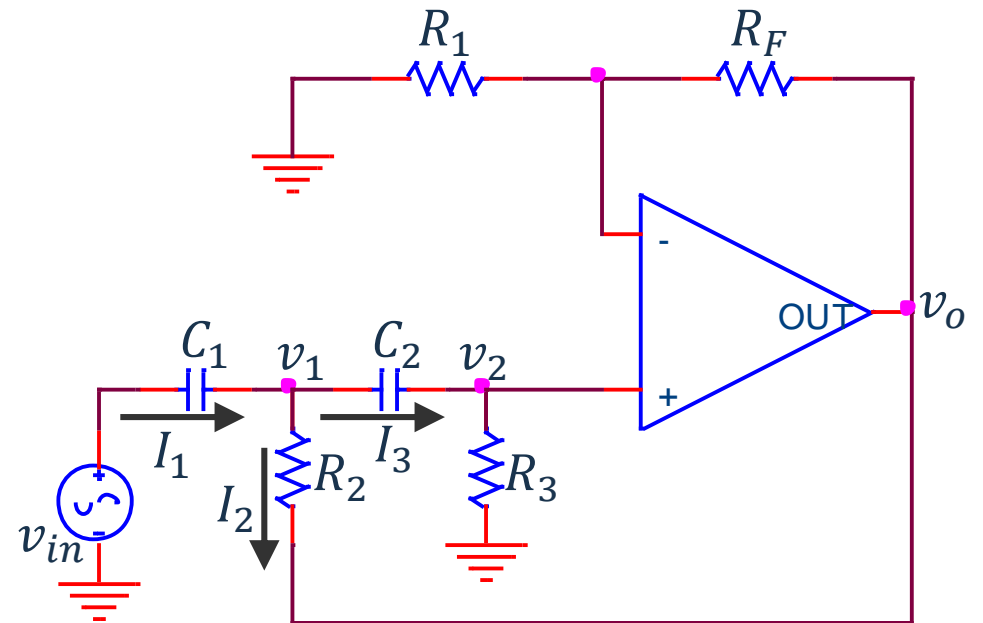

# Higher Order Filters

---

In first order filters, the gain of the filters changes at rate 20dB/decade.

Whereas, in second order the gain changes at the rate of 40dB/decade.

This means that as the order of filter is increased the stop band response of the filter approaches ideal filter response.



Higher order filter can be design by cascading first and second order filters.

For example, third order filter will require one first order and one second order filter.



Whereas, fourth order filter will require two second order filter connected in series.

# Third Order LPF


## First Order LPF

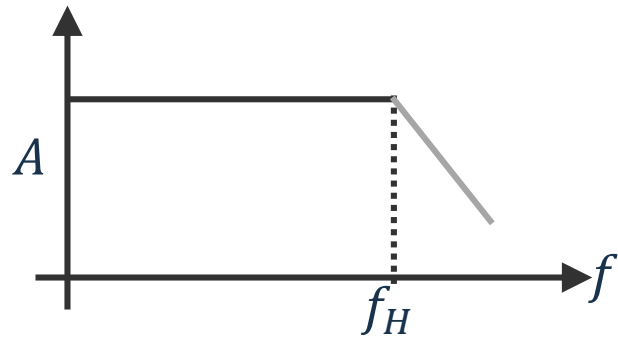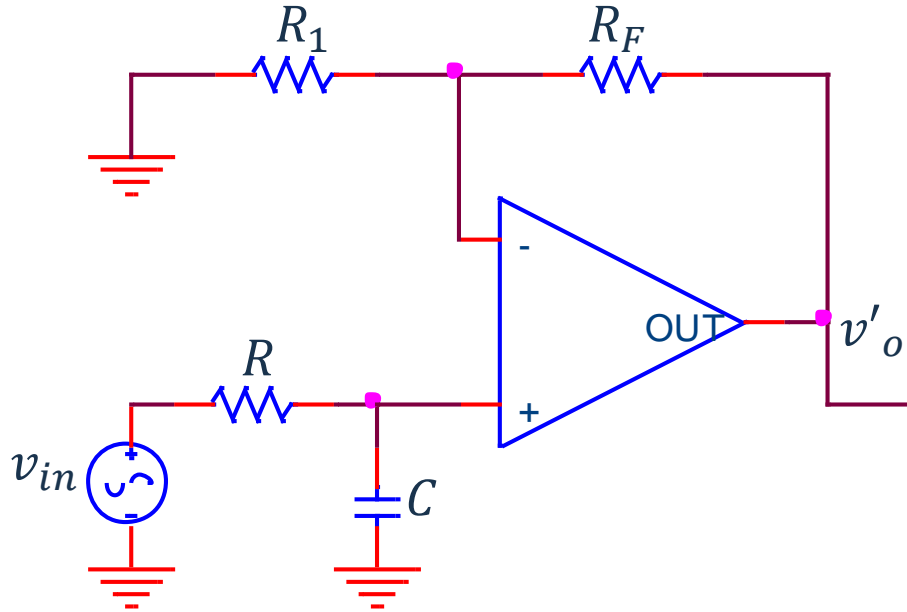

## Second Order LPF

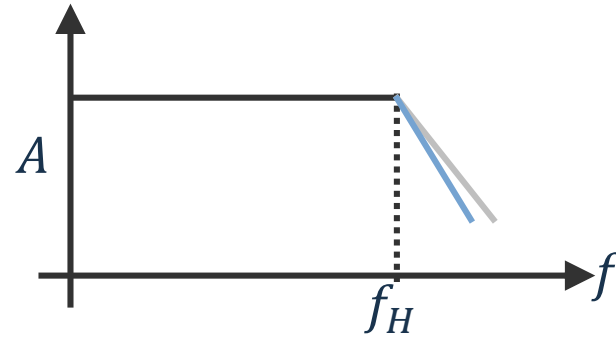
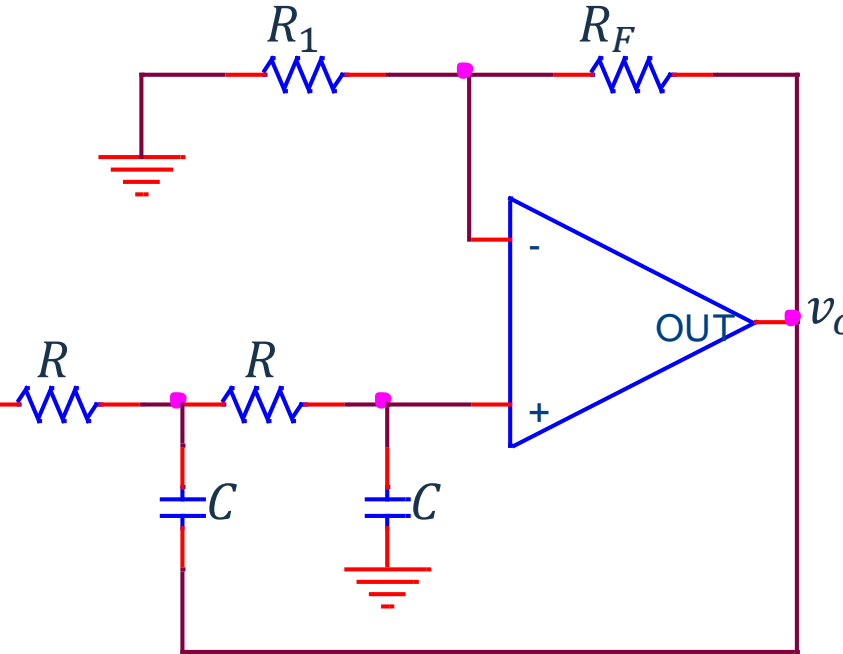


## Overall Response


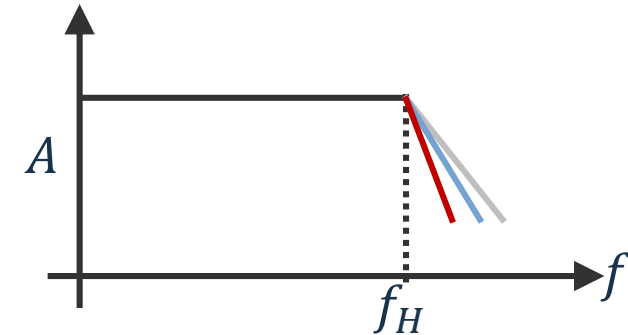


# Fourth Order LPF


## Second Order LPF

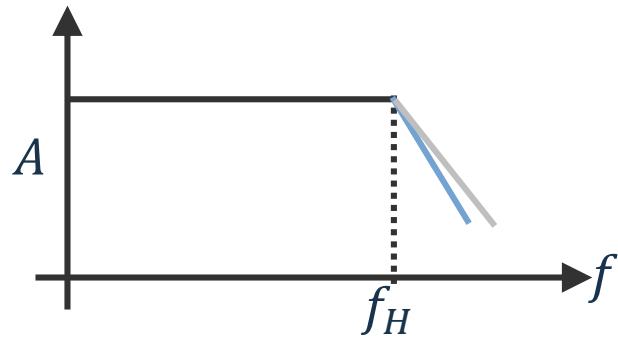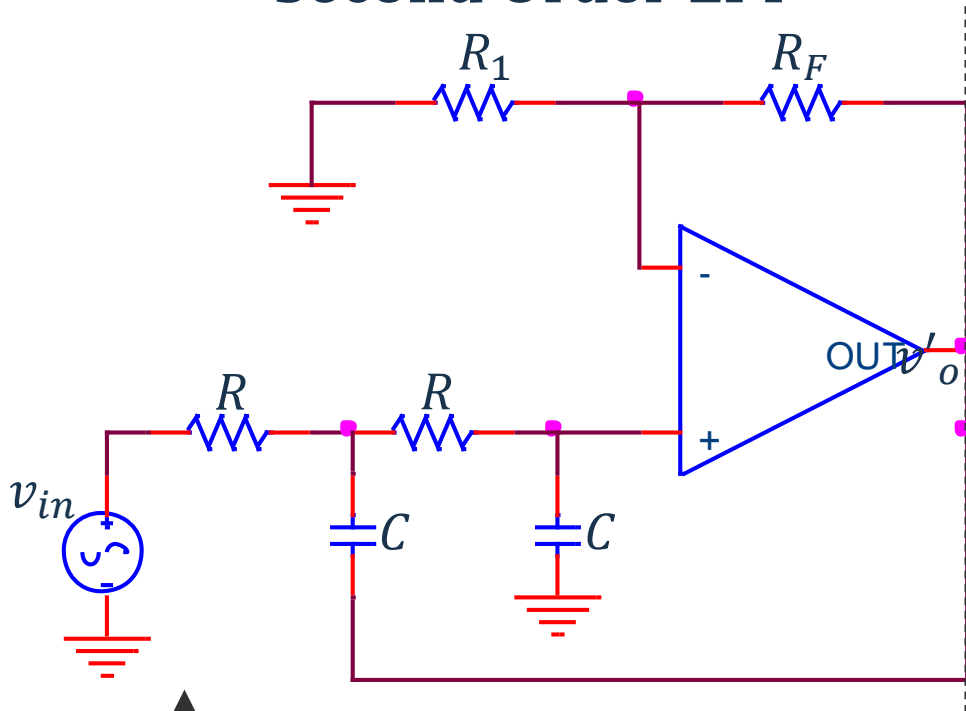

## Second Order LPF

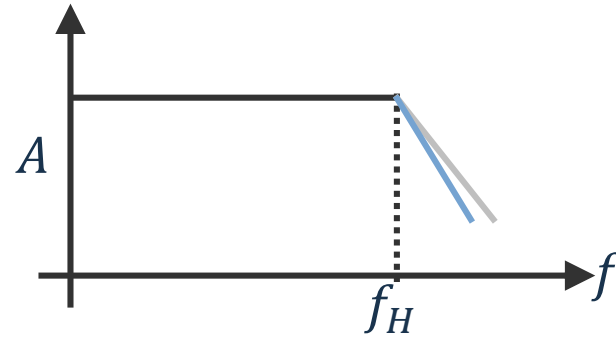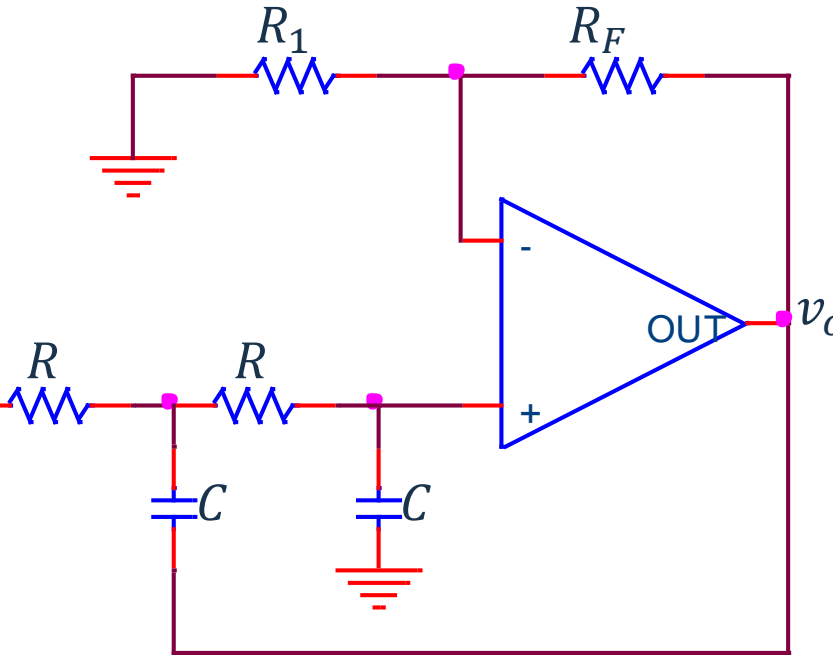

## Overall Response

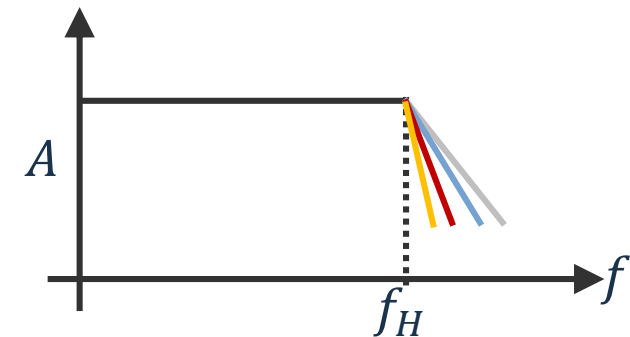

**Dr Satvir Singh**

---

# **LINEAR INTEGRATED CIRCUITS**

**Thank You**

**Do Like, Share & Subscribe**

---

*<http://DrSatvir.in>*