

**Dr Satvir Singh**

---

# **LINEAR INTEGRATED CIRCUITS**

**3-09**

**Band Pass, Band Stop & All Pass Filters**

**Do Like, Share & Subscribe**

---

*<http://DrSatvir.in>*

# Outline

---

1. Butterworth First Order High Pass Filter
2. Butterworth Second Order High Pass Filter

# First Order Butterworth HPF

The output of non-inverting amplifier is

$$v_o = \left(1 + \frac{R_F}{R_1}\right) v_1$$

Where  $v_1$  voltage is given as

$$v_1 = \frac{R}{R + \frac{1}{j2\pi fC}} v_{in} = \frac{j2\pi fCR}{1 + j2\pi fCR} v_{in}$$



Output of the non-inverting amplifier

$$v_o = \left(1 + \frac{R_F}{R_1}\right) \frac{j2\pi fRC}{1 + j2\pi fRC} v_{in}$$

$$\frac{v_o}{v_{in}} = A_F \frac{j2\pi fRC}{1 + j2\pi fRC} = A_F \frac{j(f/f_L)}{1 + j(f/f_L)}$$

Here,  $f_L = \frac{1}{2\pi RC}$  low cut-off frequency. Magnitude can be determined as

$$\left| \frac{v_o}{v_{in}} \right| = \frac{A_F (f/f_L)}{\sqrt{1 + (f/f_L)^2}}$$

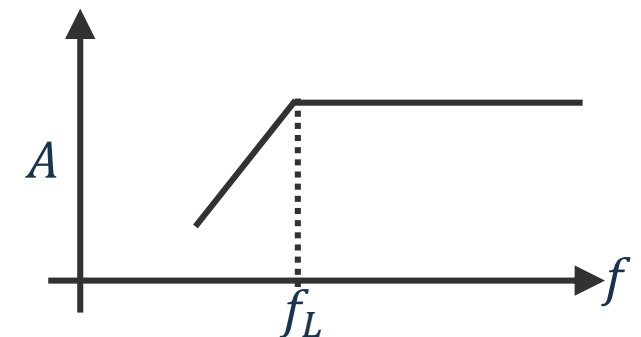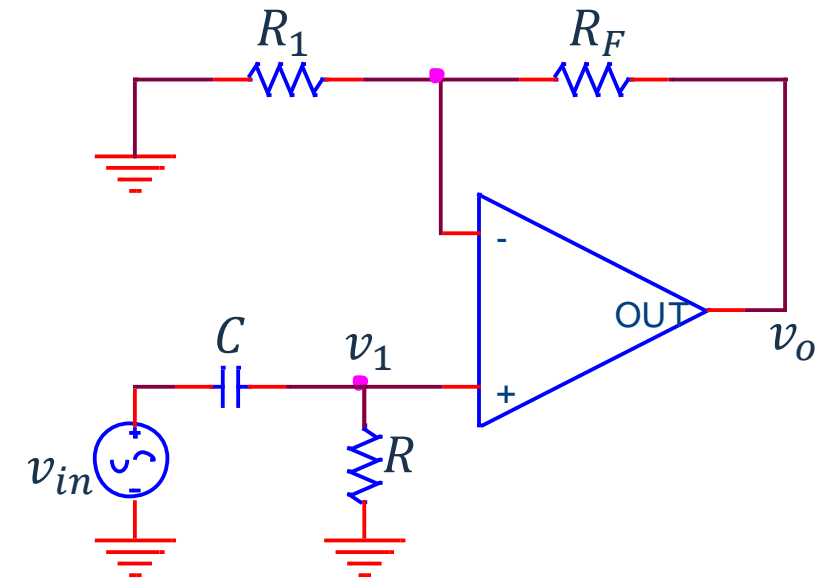



# Second Order Butterworth LPF

As we determined the cut-off frequency in Second Order Butterworth LPF, we can determine cut-off frequency of Second Order Butterworth HPF also.

$$f_L = \frac{1}{2\pi\sqrt{R_2R_3C_2C_3}}$$

For simplicity, assume  $R_2 = R_3 = R$  and  $C_2 = C_3 = C$

$$f_L = \frac{1}{2\pi RC}$$

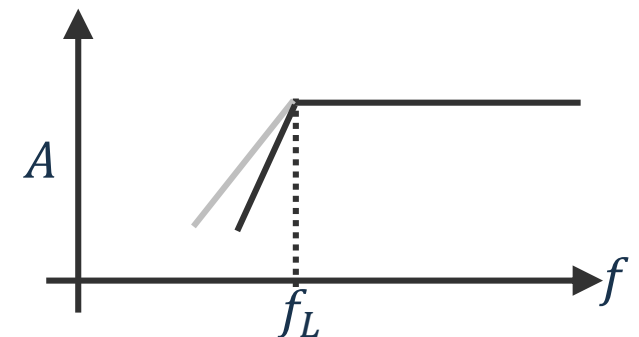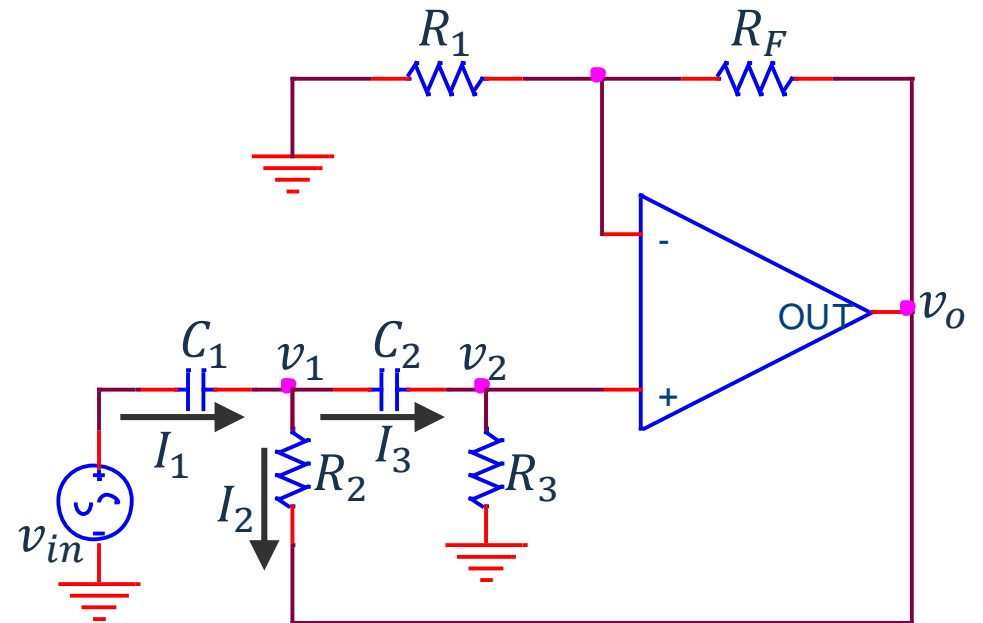

**Dr Satvir Singh**

---

# **LINEAR INTEGRATED CIRCUITS**

**Thank You**

**Do Like, Share & Subscribe**

---

*<http://DrSatvir.in>*