

Dr Satvir Singh

LINEAR INTEGRATED CIRCUITS

4-01

IC 555 Timer & Multivibrators



Do Like, Share & Subscribe

<http://DrSatvir.in>

IC555 Applications


1. Monostable Multivibrator
2. Astable Multivibrator
3. DC-DC Converters
4. Digital Logic Probes
5. Waveform Generators
6. Analog Frequency Meters & Tachometers
7. Control Devices
8. Burglar and toxic gas alarms
9. Voltage Regulators
10. Infrared Transmitters

IC555 & Pin Configuration

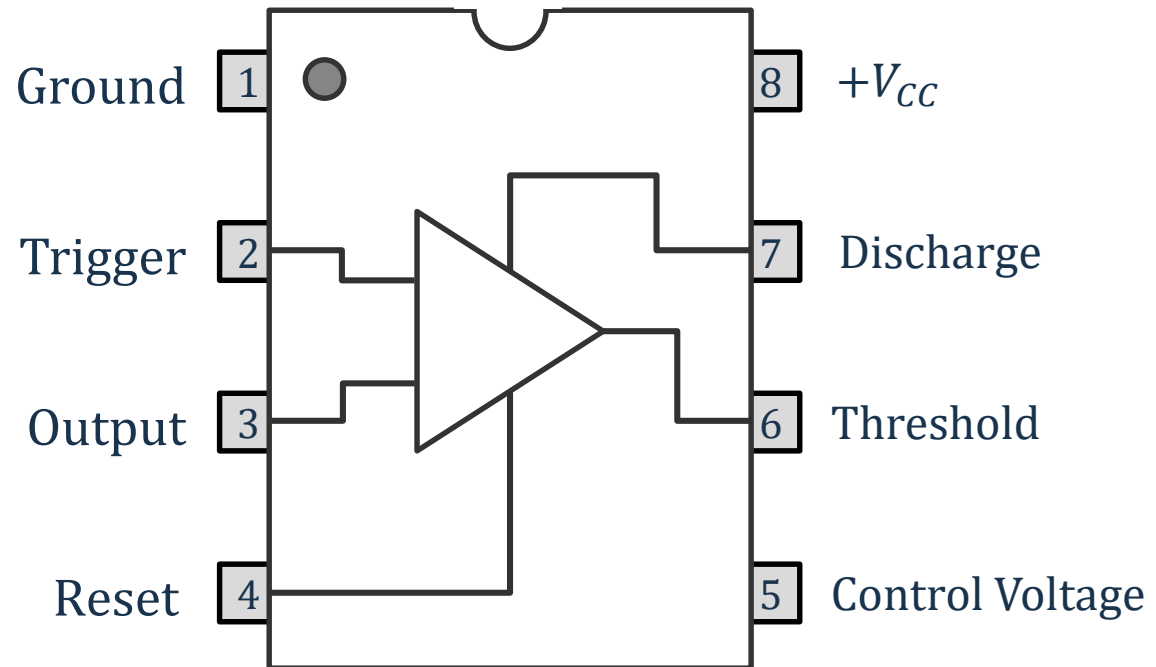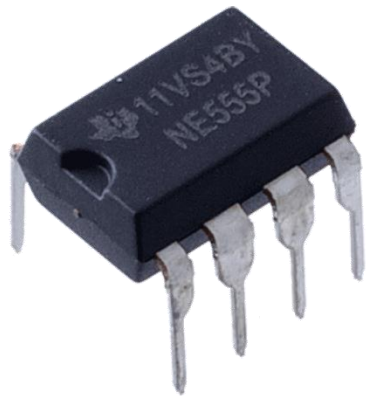



Internal Block Diagram & Features

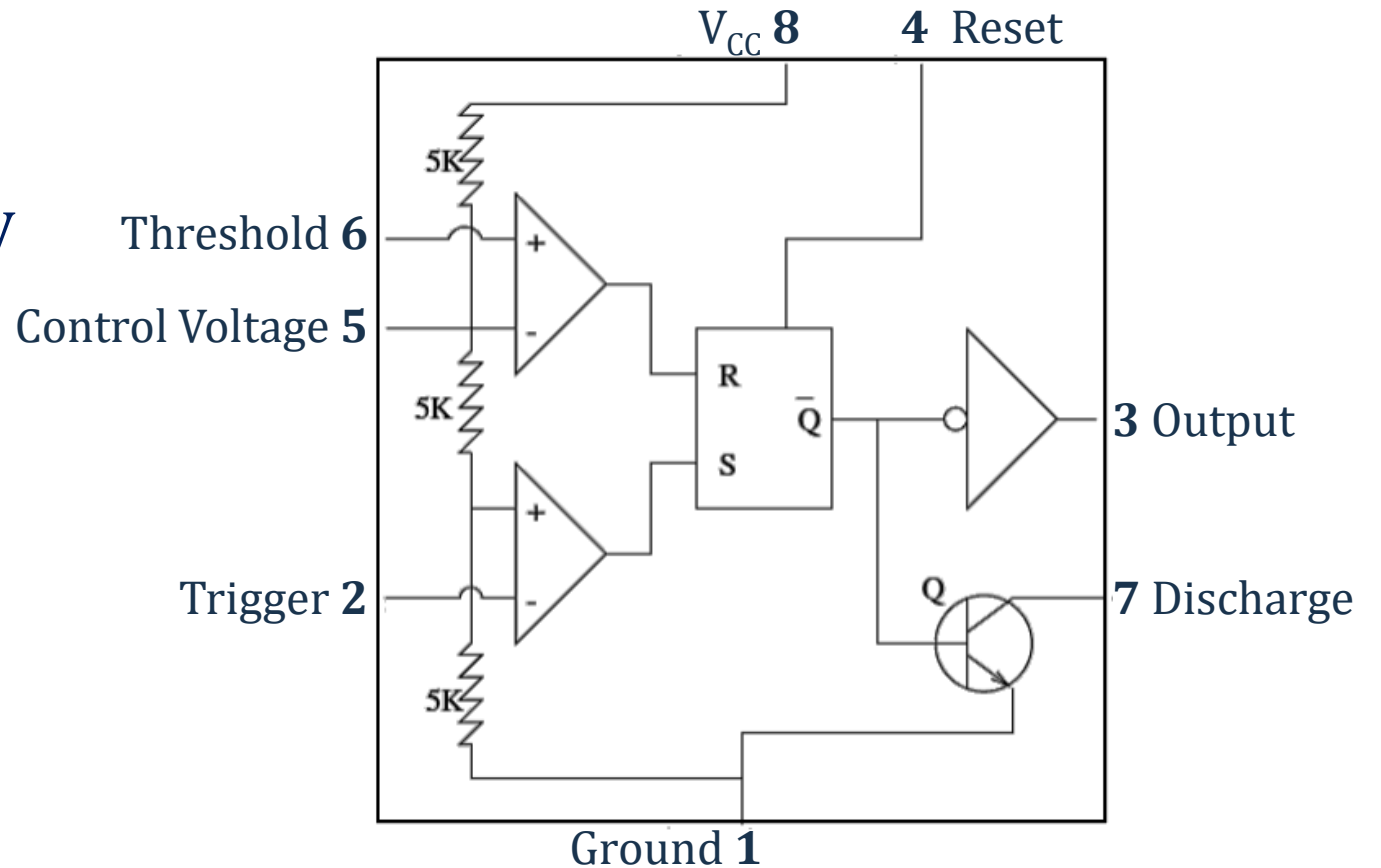- ❑ Timer IC is available in 8-pin & 14-pin
- ❑ DIP and metal can packaging
- ❑ Operating voltage range +5V to +18V
- ❑ Adjustable duty cycle
- ❑ Output can drive TTL circuitry
- ❑ Easy to use and low cost



Monostable Multivibrator

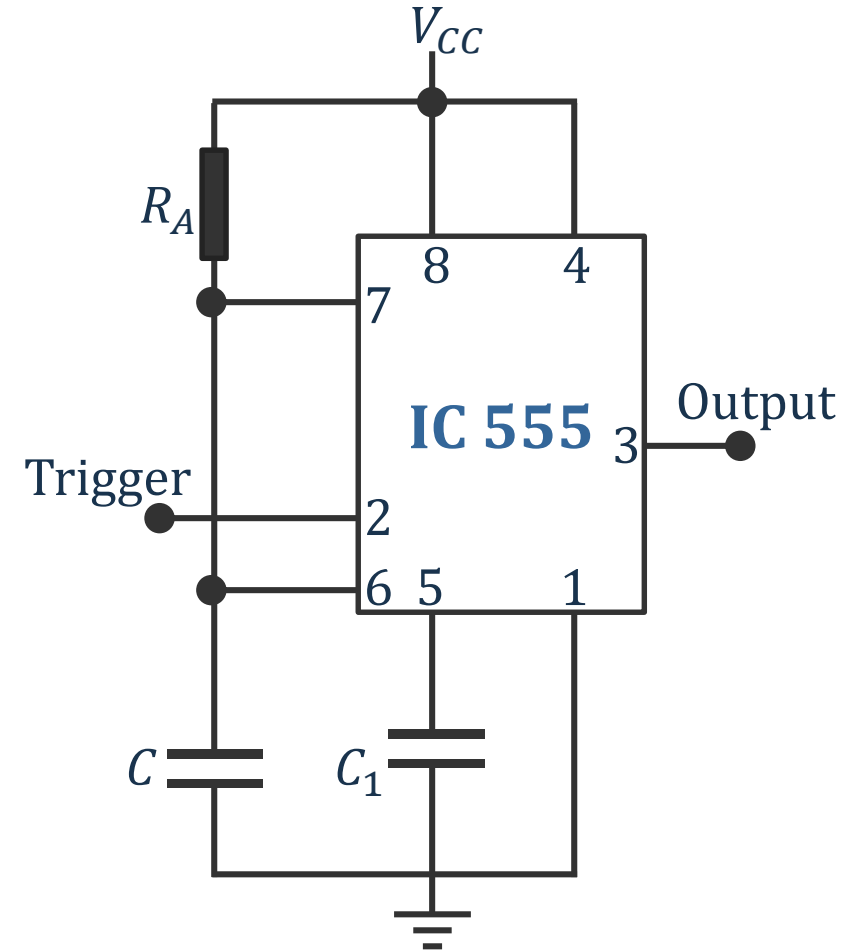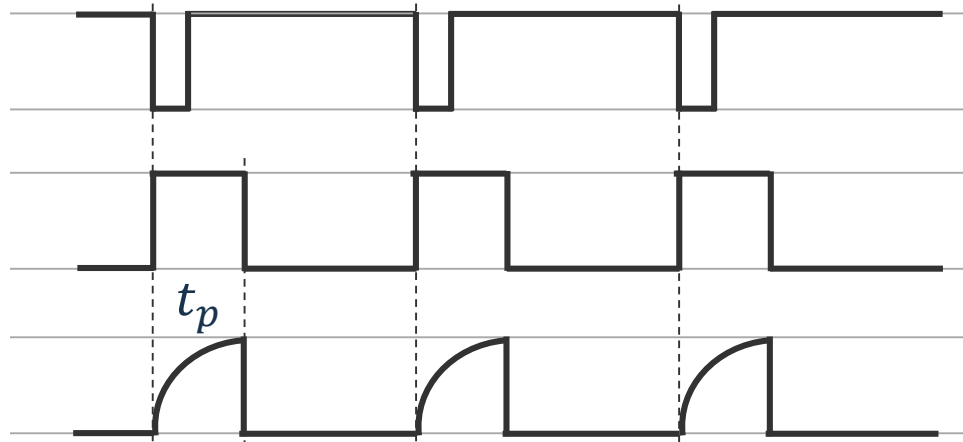- ❑ Monostable has 0 output stable state
- ❑ Generates an output pulse when triggered
- ❑ On application trigger output becomes 1
- ❑ Output pulse duration is given by $t_p = 1.1R_A C$
- ❑ After t_p output revert to 0
- ❑ Output remains 0 until triggered again



Astable Multivibrator



- ❑ Its free running Multivibrator
- ❑ Generates rectangular wave
- ❑ It does not require any external trigger
- ❑ Timings are controlled by Resistors & Capacitor

Charging time $t_c = 0.69(R_A + R_B)C$

Discharging time $t_d = 0.69R_B C$

Time period $t_p = 0.69(R_A + 2R_B)C$

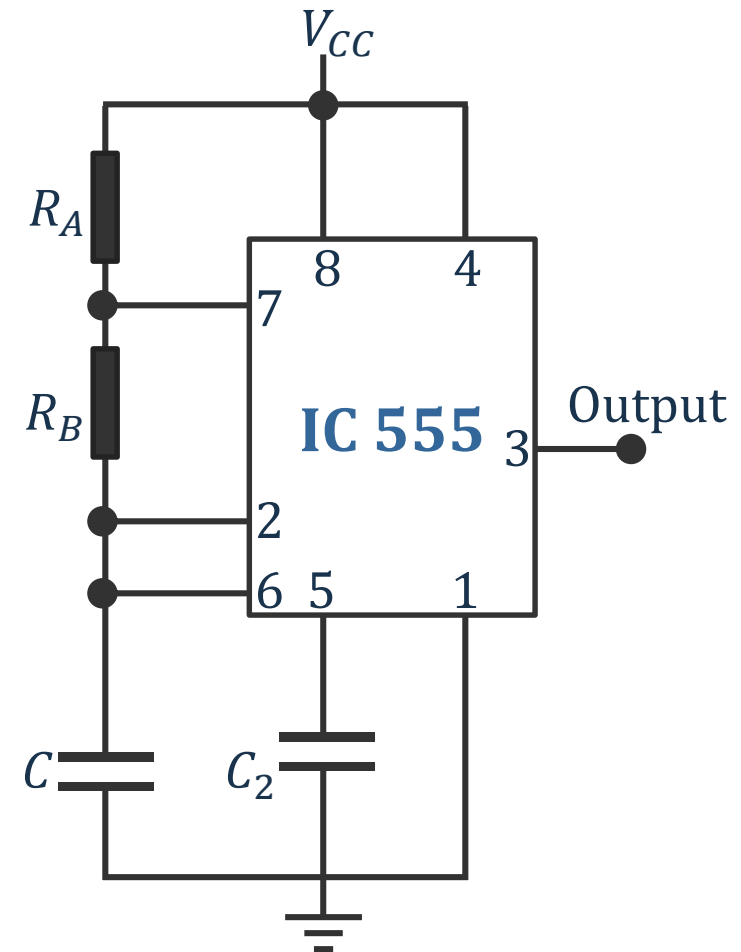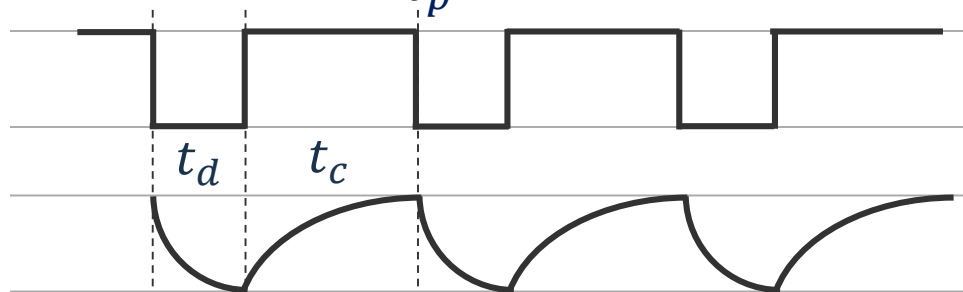Duty cycle = $\frac{t_c}{t_p} \times 100$



Dr Satvir Singh

LINEAR INTEGRATED CIRCUITS

Thank You

Do Like, Share & Subscribe

<http://DrSatvir.in>